

# Embedded Systems

## CS429 Lab1

Name: Dipean Dasgupta

ID: 202151188

Q1.

1. Implement and analyze the circuit shown in Figure 1 at three levels of abstraction using Verilog.

 


Figure 1

### Structural Level:

```
module system1(v1,v2,v3,out);  
  input v1,v2,v3;  
  output out;  
  wire w1,w2,w3;  
  
  and g1(w1,v1,v2),  
    g2(w2,v2,v3),  
    g3(w3,v3,v1);  
  or g4(out,w1,w2,w3);  
  
endmodule
```

## RTL Level:


### Module code:

```
module lab1(  
input v1,  
input v2,  
input v3,  
output out  
);  
assign  
out= (v1&v2)|(v2^v3)|(v1&v3);  
endmodule
```

### Testbench code:

```
`include "lab1.v"  
module lab1_tb;  
reg V1;  
reg V2;  
reg V3;  
wire result;  
  
lab1 u0_DUT(  
.v1(V1),  
.v2(V2),  
.v3(V3),  
.out(result)  
);  
initial begin  
$dumpfile("test_lab1.vcd");  
$dumpvars(0,lab1_tb);  
V1=0; V2=0; V3=0; #10;  
V1=0; V2=1; V3=0; #10;  
V1=1; V2=0; V3=0; #10;  
V1=1; V2=1; V3=0; #10;  
V1=0; V2=0; V3=1; #10;  
V1=0; V2=1; V3=1; #10;  
V1=1; V2=0; V3=1; #10;  
V1=1; V2=1; V3=1; #10;  
end  
endmodule
```

## Output:

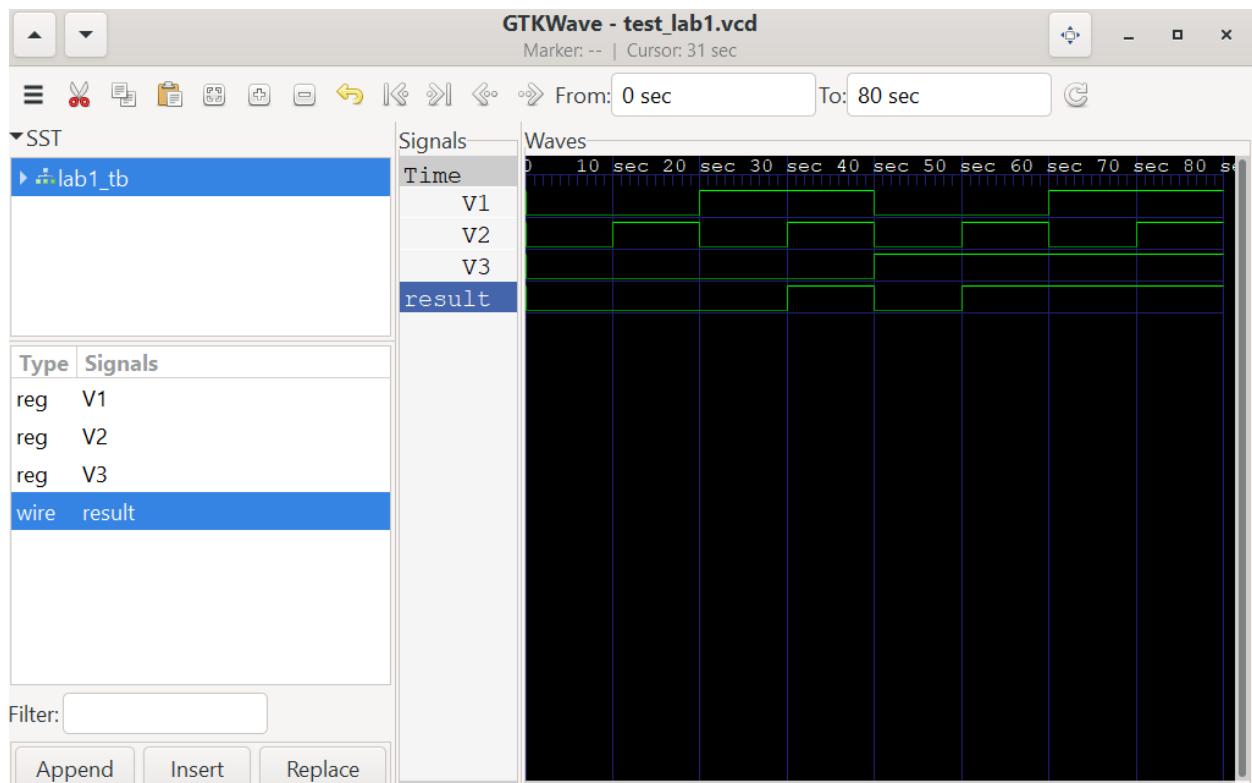

## Behavioral Level:

```
module system1(v1,v2,v3,out);  
input v1,v2,v3;  
output out;  
wire w1,w2,w3;  
  
if(v1&&v2)||v2&&v3||v3&&v1  
out=1;  
else  
out=0;  
  
endmodule
```

## Q2:

2. Using system 1 of Task 1 as instance model, implement the model shown in Figure 2.

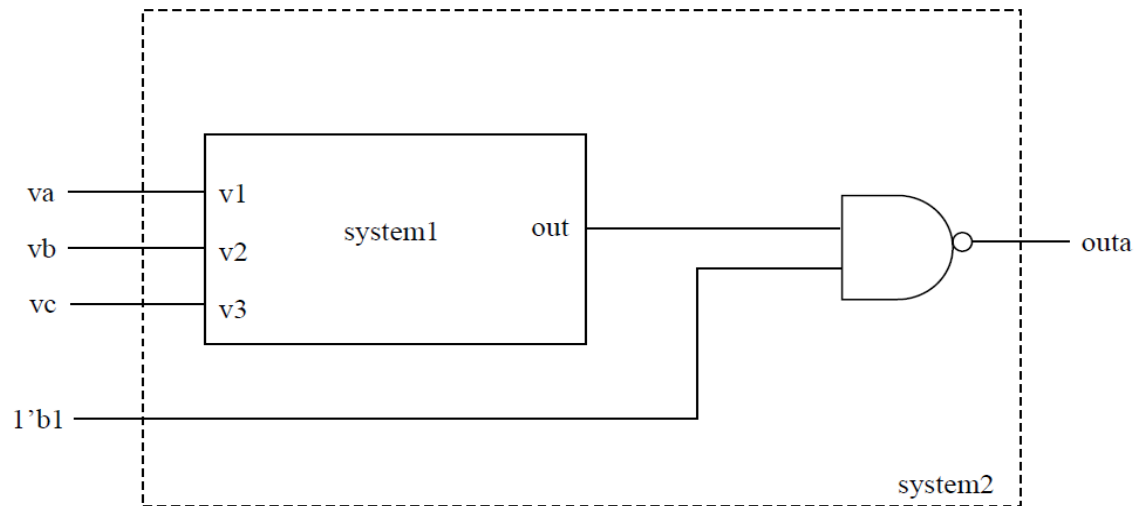


Figure 2

### Structural Level:

```
module system1(v1,v2,v3,out);
input v1,v2,v3;
output out;
wire w1,w2,w3;
and g1(w1,v1,v2),
    g2(w2,v2,v3),
    g3(w3,v3,v1);
or g4(out,w1,w2,w3);
endmodule

module system2(Va,Vb,Vc,out);
input Va,Vb,Vc;
output out;
```

```
wire=out;
system1 x1(Va,Vb,Vc,out);
nand g4(outa,out,1'b1);
endmodule
```

## EXERCISE SOLUTIONS:

**Q1. Implement half adder at three levels of abstraction.**

### Structural Level:

```
`timescale 1ns / 1ps
module system1(a,b,s,c);
input a,b;
output s,c;
xor x1(s,a,b),
and a1(c,a,b)
endmodule
```

### RTL Level:


#### Module code:

```
module halfadder(
    input a,
    input b,
    output s,
    output c
);
    assign s = a ^ b;
    assign c = a & b;
endmodule
```
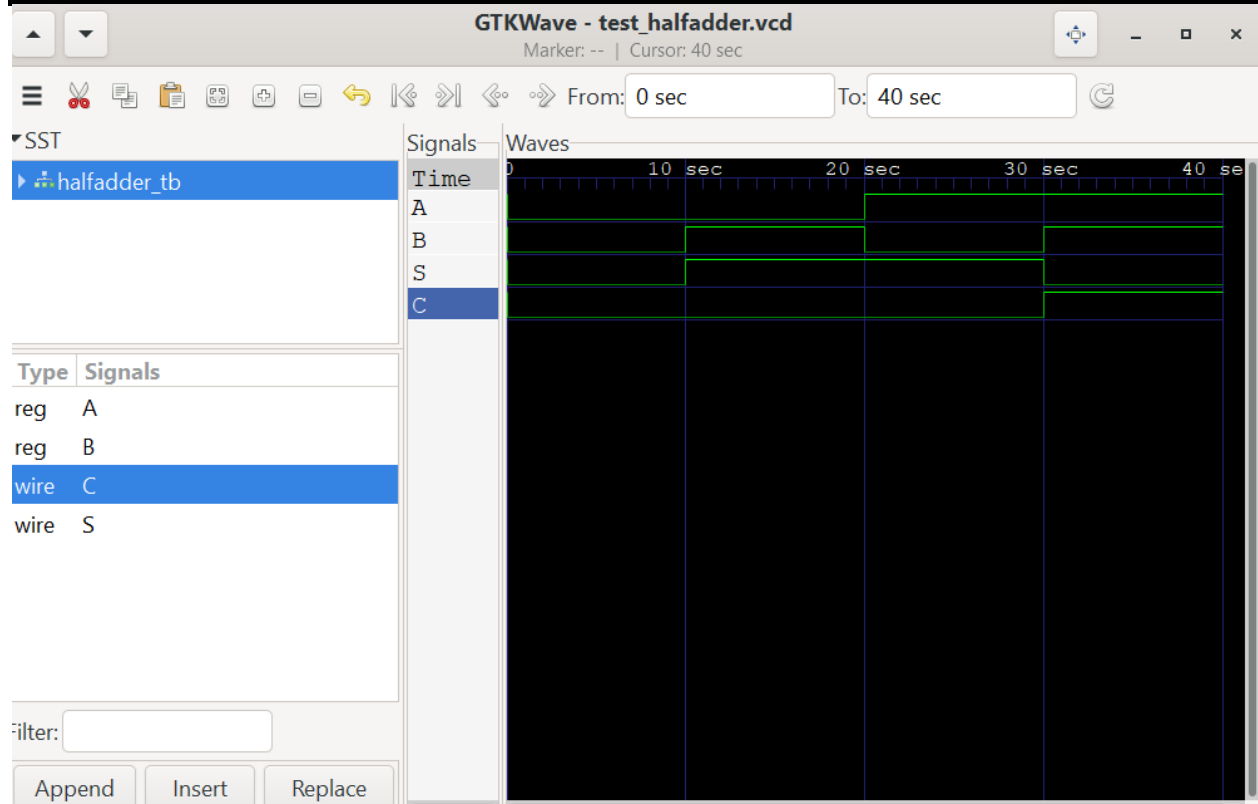
#### Testbench code:

```
`include "halfadder.v"
module halfadder_tb;
    reg A;
    reg B;
    wire S;
    wire C;
```

```
halfadder u0_DUT(  
  .a(A),  
  .b(B),  
  .s(S),  
  .c(C)  
);  
initial begin  
  $dumpfile("test_halfadder.vcd");  
  $dumpvars(0,halfadder_tb);  
  A=0; B=0; #10;  
  A=0; B=1; #10;  
  A=1; B=0; #10;  
  A=1; B=1; #10;  
  
end  
endmodule
```



### **Behavioural level:**

```
module half_adder(a,b,sum,cout);  
input a,b;  
output reg sum,cout;
```

```
always @(*)  
begin  
case ({a,b})  
2'b00: sum = 0;  
2'b01: sum = 1;  
2'b10: sum = 1;  
2'b11: sum = 0;  
default : sum = 0;  
endcase
```

```
case ({a,b})  
2'b00: cout = 0;  
2'b01: cout = 0;  
2'b10: cout = 0;  
2'b11: cout = 1;  
default : cout = 0;  
endcase  
end  
endmodule
```

### **Q2. Implement full adder at three levels of abstraction.**

#### **Structural level:**

```
module full_adder(  
input a,b,c,  
output sum,cout);  
wire w1, c1, c2, c3,out1;  
xor x1(w1, a, b);  
xor x2(sum, w1, c);  
  
and a1(c1, a, b);  
and a2(c2, b, c);  
and a3(c3, a, c);  
  
or o1(out1, c1, c2);
```

```
    or o2(cout, out1, c3);
endmodule
```

## RTL Level:

### Module Code:

```
module fulladder(
input a_i,
input b_i,
input c_i,
output sum_o,
output carry_o
);
assign
sum_o= a_i^b_i^c_i;
assign
carry_o=(a_i&b_i)|(b_i&c_i)|(c_i&a_i);

endmodule
```

### Testbench Code:

```
`include "fulladder.v"
module fulladder_tb;
reg a;
reg b;
reg c;
wire sum;
wire carry;

fulladder u0_DUT(
.a_i(a),
.b_i(b),
.c_i(c),
.sum_o(sum),
.carry_o(carry)
);
initial begin
$dumpfile("test_fulladder.vcd");
$dumpvars(0,fulladder_tb);
a=0; b=0; c=0; #10;
a=0; b=1; c=0; #10;
a=1; b=0; c=0; #10;
a=1; b=1; c=0; #10;
a=0; b=0; c=1; #10;
a=0; b=1; c=1; #10;
```




```

a=1; b=0; c=1; #10;
a=1; b=1; c=1; #10;

end
endmodule

```

## Output:

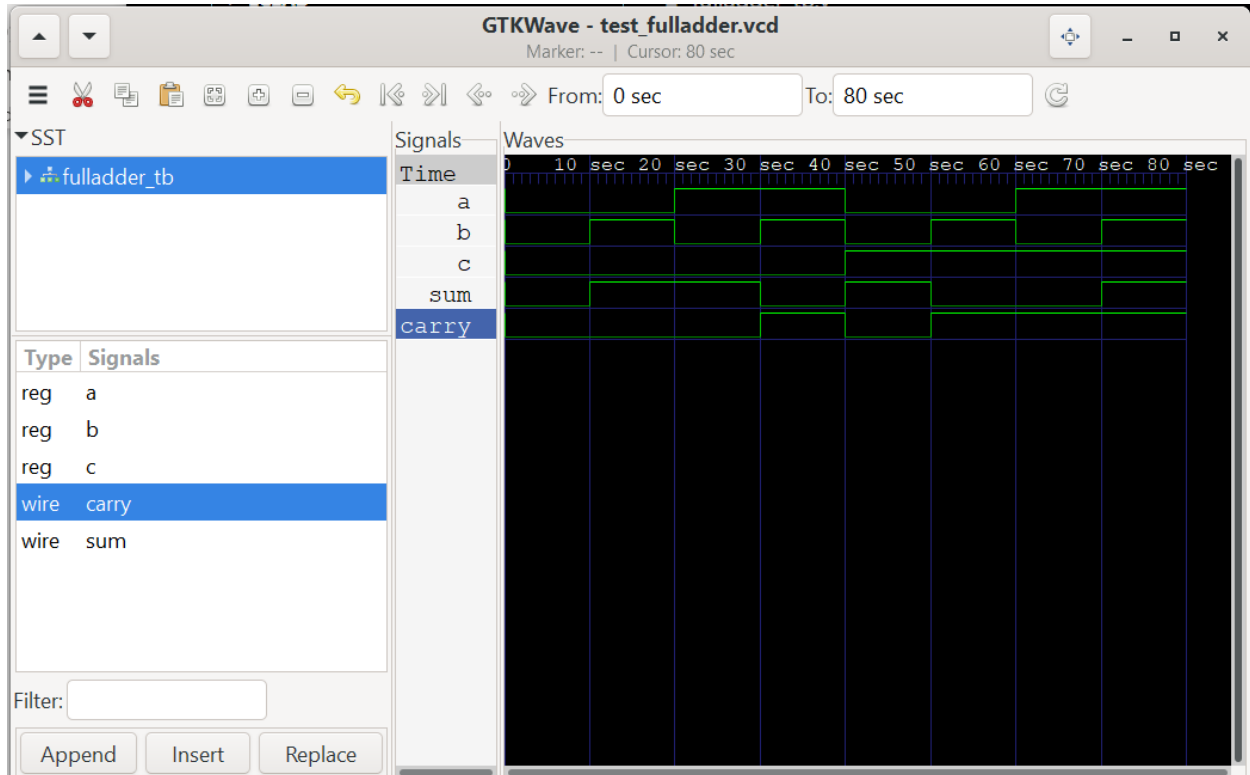

## Behavioural Level:

```

module full_adder(
input a,b,c,
output reg sum,cout);

```

```

always @(*)
begin
case ({a,b,c})
3'b000: sum = 0;
3'b001: sum = 1;
3'b010: sum = 1;
3'b011: sum = 0;
3'b100: sum = 1;
3'b101: sum = 0;
3'b110: sum = 0;
3'b111: sum = 1;

```


```

default : sum = 0;
endcase

case ({a,b,c})
3'b000: cout = 0;
3'b001: cout = 0;
3'b010: cout = 0;
3'b011: cout = 1;
3'b100: cout = 0;
3'b101: cout = 1;
3'b110: cout = 1;
3'b111: cout = 1;
default : cout = 0;
endcase
end
endmodule

```

 **Q3. Implement full adder using half adder as instance model.**



**Module Code:**

```

module full_adder(
    input a,b,cin,
    output sum,carry
);

wire c,c1,s;

half_adder ha0(a,b,s,c);

```

```
half_adder ha1(cin,s,sum,c1);
```

```
assign carry = c | c1 ;
```

```
endmodule
```

### **Testbench Code:**

```
module full_adder_tb;
```

```
reg a,b,cin;
```

```
wire sum,carry;
```

```
full_adder uut(a,b,cin,sum,carry);
```

```
initial begin
```

```
a = 0; b = 0; cin = 0;
```

```
#10
```

```
a = 0; b = 0; cin = 1;
```

```
#10
```

```
a = 0; b = 1; cin = 0;
```

```
#10
```

```
a = 0; b = 1; cin = 1;
```

```
#10
```

```
a = 1; b = 0; cin = 0;
```

```
#10
```

```
a = 1; b = 0; cin = 1;
```

```
#10
```

```
a = 1; b = 1; cin = 0;
```

```
#10
```

```
a = 1; b = 1; cin = 1;
```

```
#10
```

```
$finish();
```

```
end
```

```
endmodule
```