



# Switch Level Modeling

**Dr. Yash Agrawal**

Visiting Faculty, IIT Vadodra  
Associate Professor, DA-IICT Gandhinagar


## Introduction

## What is Switch Level Modeling...?

## Primitives

Gate Level Primitive			Switch Level Primitive		
Multi Input Gates	Multi Output Gates	Tristate Gates	Unidirectional	Bidirectional	Pull Gates
and nand or nor xor Xnor	buf not	bufif0 bufif1 notif0 notif1	nmos pmos cmos  rnmos rpmos rcmos	tran tranif0 tranif1  rtran rtranif0 rtranif1	pullup pulldown

## Switch Level Primitive

 

### Syntax


nmos <instance name> (<drain>, <source>, <gate>);

### Example

nmos n1(out1, data, control);

nmos		control			
data		0	1	x	z
	0	z	0	x (L)	x (L)
	1	z	1	x (H)	x (H)
	x	z	x	x	x
	z	z	z	z	z

L → 0 or z  
H → 1 or z

 

### Syntax

pmos <instance name> (<drain>, <source>, <gate>);


### Example

pmos n1(out2, data, control);

pmos		control			
data		0	1	x	z
	0	0	z	x (L)	x (L)
	1	1	z	x (H)	x (H)
	x	x	z	x	x
	z	z	z	z	z

# Switch Level Modeling


$$\text{out} = \overline{\text{in}}$$

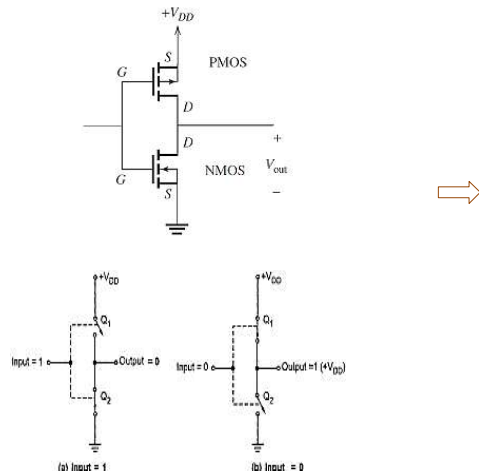

Implement using  
Switch Level Model

# Switch Level Modeling

$$\text{out} = \overline{a \cdot b}$$

 


Implement using  
Switch Level Model

# Switch Level Modeling

$$F = A + B$$

B	A	F
0	0	0
0	1	1
1	0	1
1	1	1

Implement using  
Switch Level Model

 


# Switch Level Modeling


$$F = A \cdot B$$

B	A	F
0	0	0
0	1	0
1	0	0
1	1	1

Implement using  
Switch Level Model

 


# Switch Level Modeling

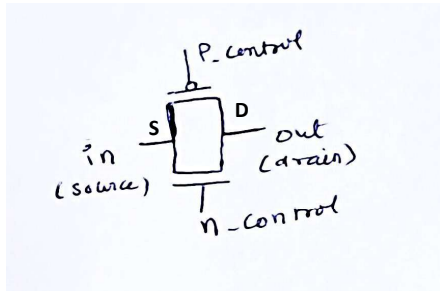


Implement using  
Switch Level Model

# Switch Level Modeling

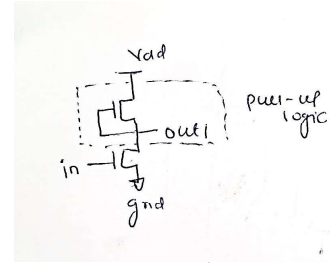


Implement using  
Switch Level Model

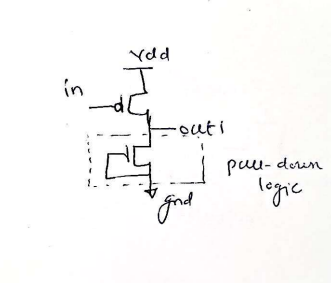


# Switch Level Modeling


## Bidirectional switches

 

tran t1(inout1, inout2);

 


tranif1 t2(inout1, inout2, control);

 


tranif0 t3(inout1, inout2, control);



# Switch Level Modeling

 

 Implement the circuits  
using  
Switch Level Model



### Usage of 'nmos' logic

  

Implement such as above  
circuits act as  
capacitor/storing element

I am available/approachable at

email: [yash\\_agrawal@iiitvadodara.ac.in](mailto:yash_agrawal@iiitvadodara.ac.in)  
[yash\\_agrawal@daiict.ac.in](mailto:yash_agrawal@daiict.ac.in)