

Indian Institute of Information Technology – Vadodara  
End-Semester Examination Autumn 2022-23  
B. Tech. (IT & CSE)  
EC-201: Digital Logic Design

Time: 3:0 hrs

Max. Marks: 75

Attempt all questions


Q. 1 Do the followings

(a)  $(110110001)_2 = (?)_{10}$

2


(b) The output of the combinational circuit given below is:

3

 

(c) In the figure shown, the output is required to be  $Y = AB + \overline{C}D$ . The gates G1 and G2 must be, respectively,

2

 

(d) Simplify the Boolean function F together with the don't-care conditions in (1) sum-of-products form and (2) product-of-sums form:

3

$$F(w, x, y, z) = \sum m(0, 1, 2, 3, 7, 8, 10) + \sum d(5, 6, 11, 15)$$

(a) A sequential circuit has two D flip-flops A and B, two inputs x and y, and one output z. The flip-flop input equations and the circuit output are as follows:

5

$$D1 = x'y + xA'$$

$$D2 = x'B + xA$$

$$z = B$$

a. Draw the logic diagram of the circuit

b. Tabulate the state table

(b) The content of a 4-bit register is initially 1101. The register is shifted six times to the right with the serial input being 101101. What is the content of the register after each shift?

5

(a) Minimize the function using K-Map  $F(A, B, C) = \sum m(1, 2, 5, 7) + \sum d(0, 4, 6)$  and what are the limitations of K-map?

5

(b) What is the minimum number of 2-input NOR gates required to implement a 4-variable function, expressed in sum-of-minterms form as


5

$f = \sum(0, 2, 5, 7, 8, 10, 13, 15)$ ? Assume that all the inputs and their complements are available.

Q. 4

(a) The logic function implemented by the circuit below is (ground implies logic 0)?

5

 

- (b) Conditionals in a continuous assignment are specified through the "?:" operator. Conditionals get inferred into a multiplexer. For example, the following is the code for a simple multiplexer 5


```
assign wire1 = (sel==1'b1) ? a : b;
```

What is the meaning of above statement and also draw the circuit diagram and output waveform?

- (c) A serial in/parallel out, 4-bit shift register initially contains all 1s. The data nibble 0111 is waiting to enter. After four clock pulses, what is the content of the register after each shift? 5

 Q. 5

A three bit pseudo random number generator is as shown in the figure. Initially, the value of output  $F(Y_2 Y_1 Y_0)$  is set to 111. The value of output  $Y$  after 8th clock cycles is ? 5



- Q. 6 (a) How to design Synchronous Counter? Give its necessary steps. 5

- (b) Design a 3-bit Asynchronous up Counter. Draw the output diagram/Timing Diagram. 5

- (c) Convert SR flip-flop to JK flip-flop and draw the state diagram of SR flip-flop and JK flip-flop. 5

- (d) Define Ring counter and Johnson counter and find usable state and no usable state. 5

- (e) A 4-bit Modulo-6 ripple counter uses J-K flip-flop. If the propagation delay of each FF is 50 ns, the maximum clock frequency that can be used is equal to \_\_\_ MHz. 5

\*\*\*\*\*END\*\*\*\*\*