

Embedded Systems

CS429 Lab8

Name: Dipean Dasgupta

ID:202151188


Task1: An embedded system has two output terminals as A and B. The signal on A and B are of 2 bits each and are to be swapped continuously. Implement the system design in Verilog HDL to execute the task.

Design code:

```
module swap(  
    output reg clk,  
    output reg [1:0]a,b  
);  
initial begin  
    clk=1'b1;  
    a=2'b00;  
    b=2'b11;  
    $dumpfile("swap.vcd");  
    $dumpvars(0,swap);  
#100 $finish;  
end  
always #5 clk = ~clk;  
always @(posedge clk )  
begin  
    b <= a;  
    a <= b;  
    $display("A=%b B=%b", a, b);  
end  
endmodule
```

OUTPUT:

```
[Running] lab9_1.v  
VCD info: dumpfile swap.vcd opened for output.  
A=00 B=11  
A=11 B=00  
A=00 B=11  
A=11 B=00  
A=00 B=11  
A=11 B=00  
A=00 B=11  
A=11 B=00  
A=00 B=11  
lab9_1.v:11: $finish called at 100 (1s)
```

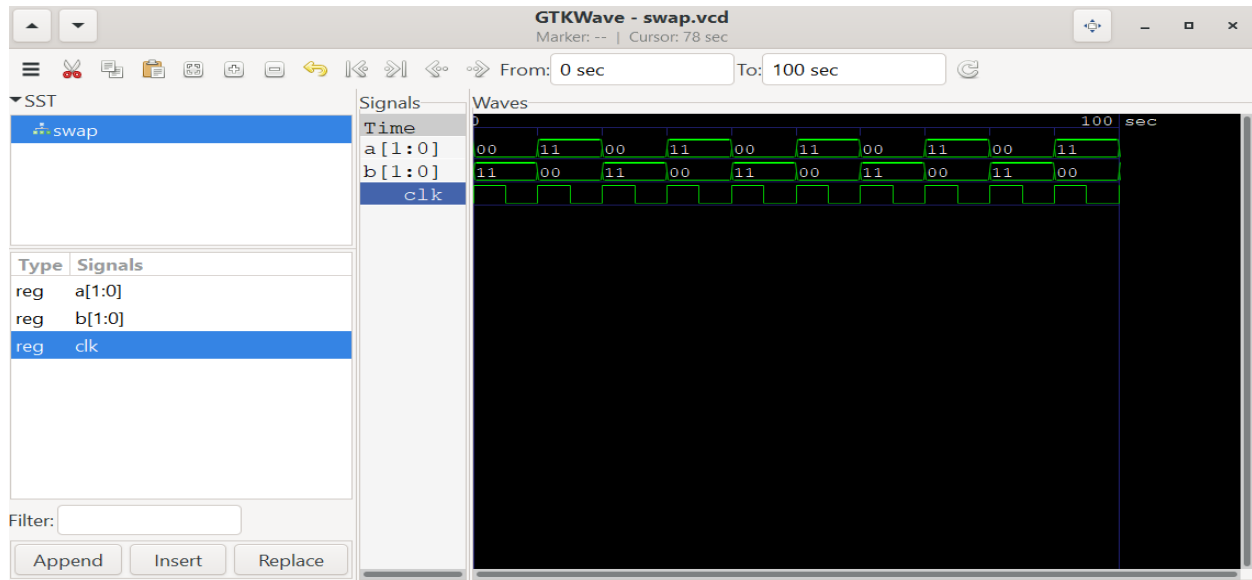

Task2: D latch and Flip-flops are often used to store the output of a system. Execute D latch and flip-flop in Verilog.

Latch:

```
`timescale 1ns/1ns
module latch(
    input d,en,
    output q
);
assign q=en?d;q;

endmodule

module latch_tb;
    parameter CLK_PERIOD = 10;
    reg d;
    reg en;
    reg clk;
    wire q;

    latch uut (
        .d(d),
        .en(en),
        .q(q)
    );
    always #((CLK_PERIOD)/2) clk = ~clk;
    // Stimulus
    initial begin
        d = 0; en = 0; clk = 0;
```

```

    #10 d = 1;
    #10 en = 1;
    #10 d = 0;
    #10 en = 0;
    #10 d = 1;
    #10 en = 1;
    #10;
    $finish;
end
always @(posedge clk) begin
    $display("q = %b", q);
end
endmodule

```

OUTPUT:

```

[Running] lab9_2A.v
q = x
q = x
q = 1
q = 0
q = 0
q = 0
q = 1
lab9_2A.v:38: $finish called at 70 (1ns)
[Done] exit with code=0 in 0.298 seconds

```

D Flipflop:

```

module d_flipflop (
    input wire clk,
    input wire reset,
    input wire d,
    output reg q
);
    always @(posedge clk or posedge reset) begin
        if (reset)
            q <= 1'b0;
        else
            q <= d;
        end
    end
endmodule

```

```

module d_flipflop_tb;
    reg clk;
    reg reset;
    reg d;
    wire q;
    d_flipflop uut (
        .clk(clk),
        .reset(reset),
        .d(d),
        .q(q)
    );
    initial begin
        clk = 0;
        reset = 1;
        d = 0;
        #10 reset = 0;
        #10 d = 1;
        #10 d = 0;
        #10 d = 1;
        #10 $finish;
    end
    always begin
        #5 clk = ~clk;
    end
    always @(posedge clk) begin
        $display("Time %0t: clk = %b, reset = %b, d = %b, q = %b", $time, clk, reset,
d, q);
    end
endmodule

```

OUTPUT:

```

[Running] lab9_2B.v
Time 5: clk = 1, reset = 1, d = 0, q = 0
Time 15: clk = 1, reset = 0, d = 0, q = 0
Time 25: clk = 1, reset = 0, d = 1, q = 0
Time 35: clk = 1, reset = 0, d = 0, q = 1
Time 45: clk = 1, reset = 0, d = 1, q = 0
lab9_2B.v:39: $finish called at 50 (1s)
[Done] exit with code=0 in 0.296 seconds

```

Task3: (i) Design D Flip-flop

(a) With synchronous reset

(b) With asynchronous reset and preset with reset having highest priority

(ii) Write a test-bench to check functionality of the module in 3(i).

a)

Code:

```
module flipflop(  
    input d,clk,r,  
    output reg q  
);  
always @(posedge clk or posedge r) begin  
    if(r)  
        q<=1'b0;  
    else  
        q<=d;  
end  
endmodule  
module flipflop_tb;  
    reg clk;  
    reg r;  
    reg d;  
    wire q;  
  
    flipflop uut (  
        .d(d),  
        .clk(clk),  
        .r(r),  
        .q(q)  
    );  
  
    initial begin  
        clk = 0;  
        forever #5 clk = ~clk;  
    end  
    initial begin  
        r = 0;  
        d = 0;  
        #10 d = 1;  
        #10 d = 0;  
        #10 d = 1;  
        #10 r = 1;  
        #10 r = 0;
```

```

    #10 $finish;
end

always @(posedge clk) begin
    $display("Time %0t: clk = %b, r = %b, d = %b, q = %b", $time, clk, r, d, q);
end
endmodule

```

OUTPUT:

```

[Running] lab9_3A.v
Time 5: clk = 1, r = 0, d = 0, q = x
Time 15: clk = 1, r = 0, d = 1, q = 0
Time 25: clk = 1, r = 0, d = 0, q = 1
Time 35: clk = 1, r = 0, d = 1, q = 0
Time 45: clk = 1, r = 1, d = 1, q = 0
Time 55: clk = 1, r = 0, d = 1, q = 0
lab9_3A.v:37: $finish called at 60 (1s)
[Done] exit with code=0 in 0.306 seconds

```

b) Code:

```

module flipflops(
    input d, clk, r ,pr,
    output reg q
);
    always @(posedge clk)
    begin
        if (r == 1'b1)
            q <= 1'b0;
        else if (pr == 1'b1)
            q <= 1'b1;
        else
            q <= d;
        end
    endmodule

module flipflops_tb;
    reg clk;
    reg r;
    reg pr;
    reg d;
    wire q;
    flipflops uut (
        .d(d),

```

```

        .clk(clk),
        .r(r),
        .pr(pr),
        .q(q)
    );
    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end
    initial begin
        r = 0;
        pr = 0;
        d = 0;
        #10 d = 1;
        #10 d = 0;
        #10 pr = 1;
        #10 r = 1;
        #10 r = 0;
        #10 pr = 0;
        #10 $finish;
    end
    always @(posedge clk) begin
        $display("Time %0t: clk = %b, r = %b, pr = %b, d = %b, q = %b", $time, clk,
r, pr, d, q);
    end
endmodule

```

OUTPUT:

```

[Running] lab9_3B.v
Time 5: clk = 1, r = 0, pr = 0, d = 0, q = x
Time 15: clk = 1, r = 0, pr = 0, d = 1, q = 0
Time 25: clk = 1, r = 0, pr = 0, d = 0, q = 1
Time 35: clk = 1, r = 0, pr = 1, d = 0, q = 0
Time 45: clk = 1, r = 1, pr = 1, d = 0, q = 1
Time 55: clk = 1, r = 0, pr = 1, d = 0, q = 0
Time 65: clk = 1, r = 0, pr = 0, d = 0, q = 1
lab9_3B.v:44: $finish called at 70 (1s)
[Done] exit with code=0 in 0.238 seconds

```

4. For some application in Embedded design, a few clock pulses (clk, clka, clkb, clkc) are needed as shown in Fig. 1. Generate these clock pulses using behavioral modeling (without using delay assignments).

 


Fig. 1. Clock signals.

Code:

```
module clk_generator (  
    input clk,  
    output reg clka, clkb, clkc  
);  
  
Initial begin  
    clka = 1'b0;  
    clkb = 1'b0;  
    clkc = 1'b0;  
    $dumpfile("clk_generator.vcd");  
    $dumpvars(0, clk_generator);  
end  
  
always @(posedge clk)  
    clka <= ~clka;  
always @(posedge clka)  
    clkb <= ~clkb;  
always @(posedge clkb)  
    clkc <= 1'b1;  
always @(negedge clka)  
    clkc <= 1'b0;  
endmodule  
  
`timescale 1ns/1ns  
module tb_clk_generator;  
    reg clk;  
    wire clka, clkb, clkc;  
    clk_generator uut (  
        .clk(clk),  
        .clka(clka),  
        .clkb(clkb),  
        .clkc(clkc)  
    );  
    initial begin  
        clk = 0;  
        forever #5 clk = ~clk;  
    end  
endmodule
```



```

end
initial begin
    #10;
    $display("Initial values: clka=%b, clkb=%b, clkc=%b", clka, clkb, clkc);
    #20;
    $display("After 20 cycles: clka=%b, clkb=%b, clkc=%b", clka, clkb, clkc);
    #30;
    $display("After 30 cycles: clka=%b, clkb=%b, clkc=%b", clka, clkb, clkc);
    #40;
    $display("After 40 cycles: clka=%b, clkb=%b, clkc=%b", clka, clkb, clkc);
    #50;
    $display("After 50 cycles: clka=%b, clkb=%b, clkc=%b", clka, clkb, clkc);
    #10;
    $finish;
end
endmodule

```

OUTPUT:

```

[Running] lab9_4.v
VCD info: dumpfile clk_generator.vcd opened for output.
Initial values: clka=1, clkb=1, clkc=1
After 20 cycles: clka=1, clkb=0, clkc=0
After 30 cycles: clka=0, clkb=1, clkc=0
After 40 cycles: clka=0, clkb=1, clkc=0
After 50 cycles: clka=1, clkb=0, clkc=0
lab9_4.v:59: $finish called at 160 (1ns)
[Done] exit with code=0 in 0.237 seconds

```

