

Embedded Systems

CS429 Lab2

Name: Dipean Dasgupta

ID:202151188

Task1 Solution:

Module code:

```
`timescale 1ns/1ps
module xor_gate(
input a,b,
output out
);
wire d,e,f,g;
not_gate n1(a,d);
not_gate n2(b,e);
and_gate a1(a,e,f);
and_gate a2(b,d,g);
or_gate o1(f,g,out);
endmodule

module not_gate(
    input a,
    output o
);
    assign #0.03 o = ~a;
endmodule

module and_gate(
    input a,
    input b,
    output o1
);
    assign #1 o1 = a & b;
endmodule

module or_gate(
    input a,
    input b,
    output o2
);
    assign #1.5 o2 = a | b;
endmodule
```

TestBench Code:

```
`include "lab2_1.v"
module lab2_1tb();
reg a;
reg b;
wire o;


xor_gate x1(.a(a),.b(b),.out(o));

initial begin
$dumpfile("lab2_1test.vcd");
$dumpvars(0, lab2_1tb);

    #0  a = 0;  b = 0;
    #10 a = 0;  b = 1;
    #10 a = 1;  b = 0;
    #10 a = 1;  b = 1;
    #10 $finish;
end

endmodule
```

OUTPUT:

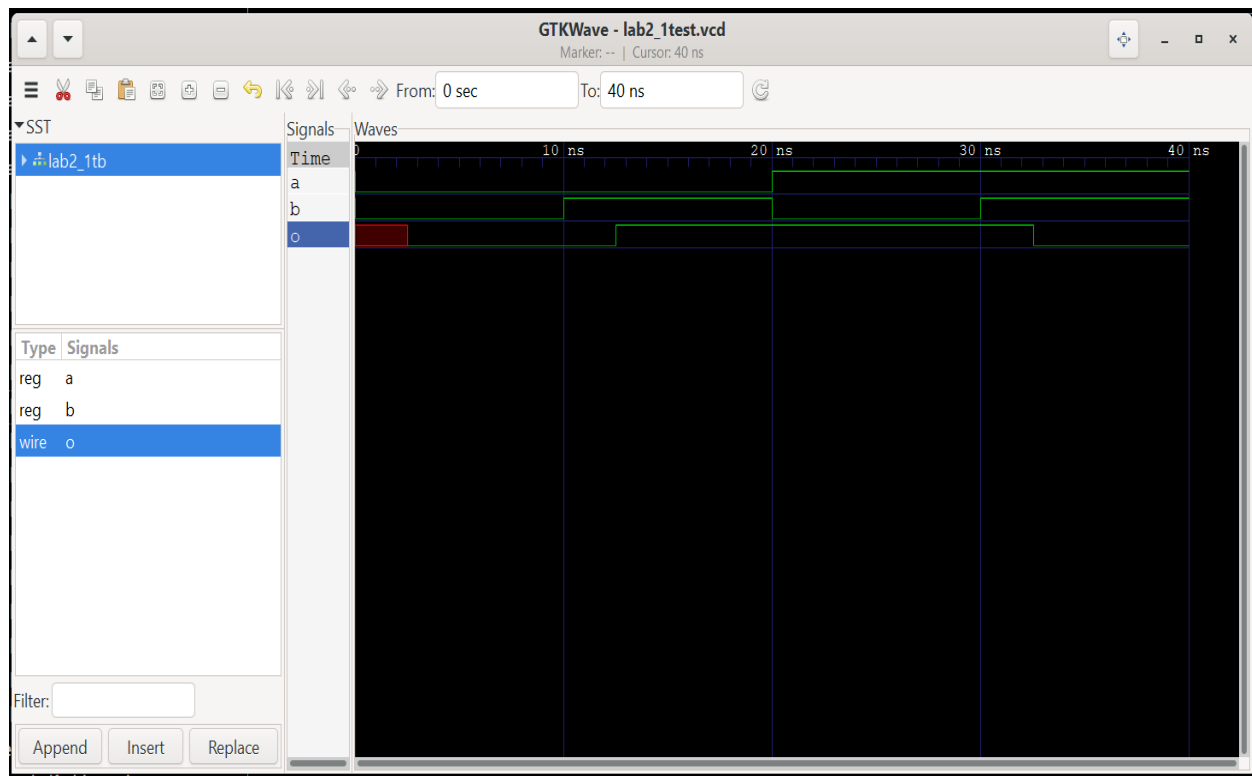


Task2a Solution:

Gate primitive

Module and Testbench Code:

```
module nor_gate(  
    input a,  
    input b,  
    output y  
);  
    assign y = ~(a | b);  
endmodule  
  
module nor_gate_tb;  
    reg a;  
    reg b;  
    wire y;  
    nor_gate uut(  
        .a(a),  
        .b(b),  
        .y(y)  
    );  
  
    initial begin  
        $dumpfile("nor_gate_tb.vcd");  
        $dumpvars(0, nor_gate_tb);  
        //$monitor($time, " a=%b b=%b y=%b", a, b, y);  
  
        #0 a=0; b=0;  
        #10 a=0; b=1;  
        #10 a=1; b=0;  
        #10 a=1; b=1;  
        $finish;  
    end  
endmodule
```

OUTPUT:

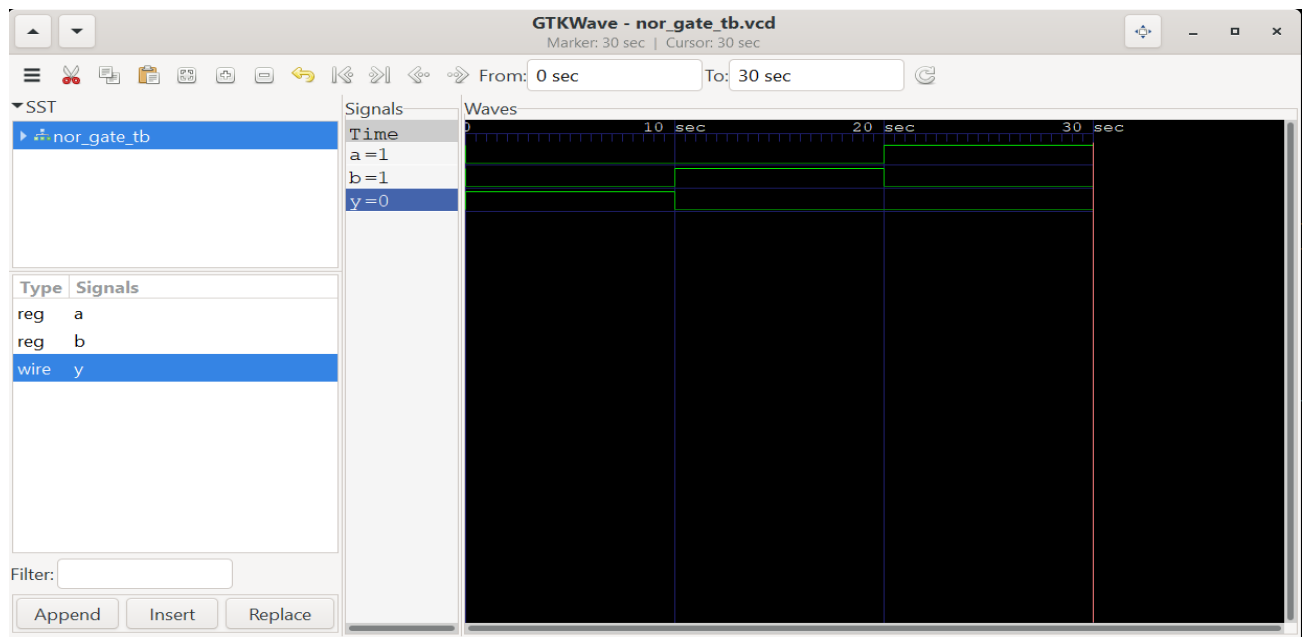


User Defined Primitive

Module and Testbench Code:


```
primitive lab2_2(  
  output o,  
  input a,  
  input b  
);  
  table  
    0 0: 1;  
    0 1: 0;  
    1 0: 0;  
    1 1: 0;  
  endtable  
endprimitive  
  
module lab2_2tb;  
  wire o;  
  reg a;  
  reg b;  
  lab2_2 u0_DUT(  
    .o(o),  
    .a(a),  
    .b(b)  
  );  
);
```

```
initial begin
$dumpfile("test_lab2_2.vcd");
$dumpvars(0,lab2_2tb);
a=0; b=0; #10;
a=0; b=1; #10;
a=1; b=0; #10;
a=1; b=1; #10;
end
endmodule
```

OUTPUT:

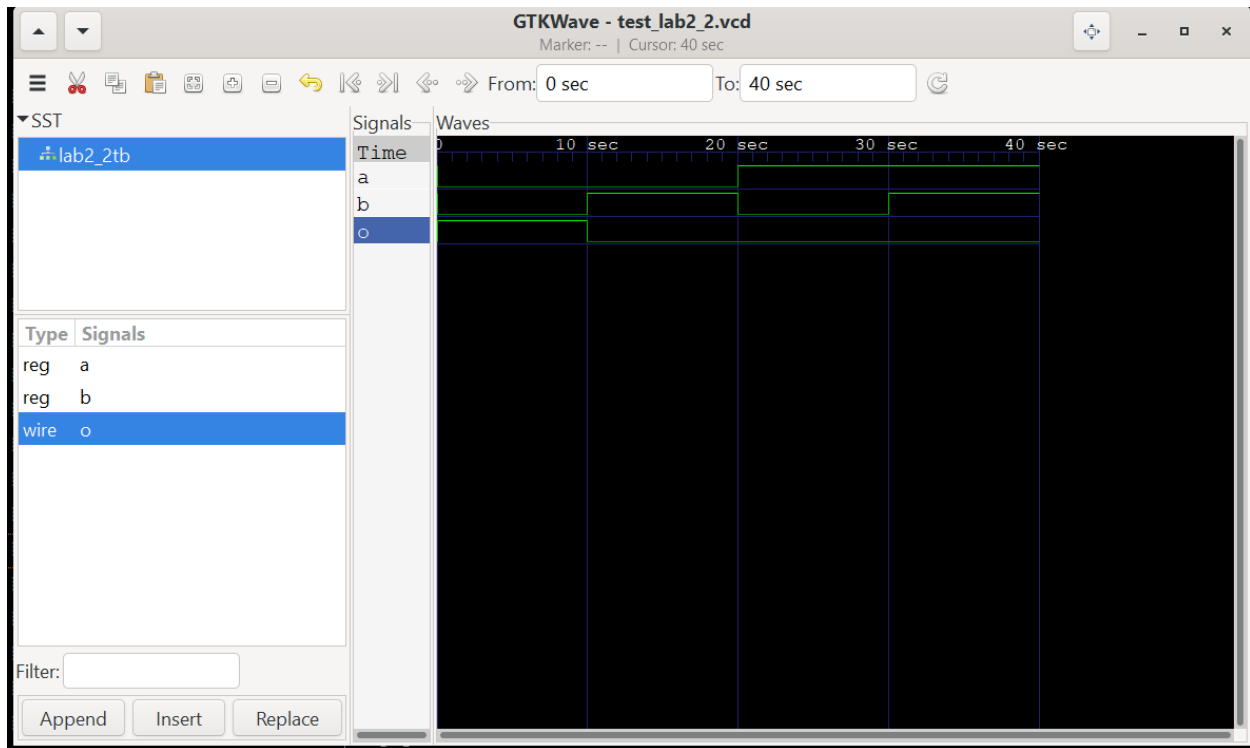

Task2b Solution ()

 

XOR using NOR gates

Module and Testbench Code:

```
primitive nor_gate (
output Y,
input A,
input B);
    table
        0 0 : 1;
        0 1 : 0;
        1 0 : 0;
        1 1 : 0;
    endtable
endprimitive

// UDP definition for XOR gate using NOR gates
module xor_gate (output Y, input A, input B);
    wire n1, n2, n3,n4;
    nor_gate u1 (.Y(n1), .A(A), .B(B));
    nor_gate u2 (.Y(n2), .A(A), .B(n1));
    nor_gate u3 (.Y(n3), .A(B), .B(n1));
    nor_gate u4 (.Y(n4), .A(n2), .B(n3));
    nor_gate u5 (.Y(Y), .A(n4), .B(n4));
endmodule


module exor_gatetb;
    reg A, B;
    wire Y;
    // Instantiate the XOR gate
    xor_gate uut (
        .Y(Y),
        .A(A),
        .B(B)
```

```

);
initial begin
    $dumpfile("test_exor_gate.vcd");
    $dumpvars(0, exor_gatetb);
    A = 0; B = 0; #10;
    A = 0; B = 1; #10;
    A = 1; B = 0; #10;
    A = 1; B = 1; #10;
    $finish;
end
endmodule

```

OUTPUT:

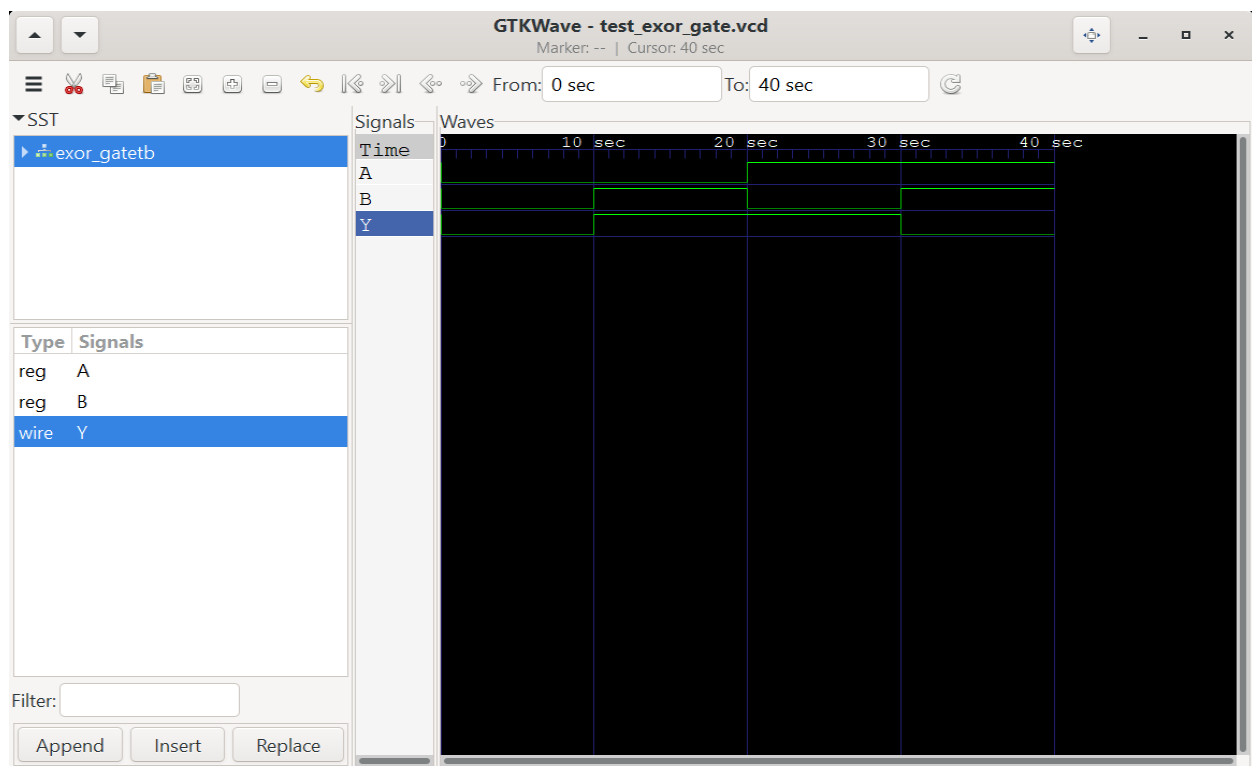

Task3 Solution:

RTL Level:

Module and Testbench Code:

```

module lab3(
    input a,
    input b,
    input c,
    input d,
    output y

```

```

    );
    assign y = (~(a & b) | (c & d)) ^ ((a & b) | ~(c & d));
endmodule

module lab3_tb;
reg a;
reg b;
reg c;
reg d;
wire y;


lab3 uut(.a(a),
        .b(b),
        .c(c),
        .d(d),
        .y(y));

initial begin
    $dumpfile("lab3_tb.vcd");
    $dumpvars(0, lab3_tb);
    #0 a=0; b=0; c=0; d=0;
    #10 a=0; b=0; c=0; d=1;
    #10 a=0; b=0; c=1; d=0;
    #10 a=0; b=0; c=1; d=1;
    #10 a=0; b=1; c=0; d=0;
    #10 a=0; b=1; c=0; d=1;
    #10 a=0; b=1; c=1; d=0;
    #10 a=0; b=1; c=1; d=1;
    #10 a=1; b=0; c=0; d=0;
    #10 a=1; b=0; c=0; d=1;
    #10 a=1; b=0; c=1; d=0;
    #10 a=1; b=0; c=1; d=1;
    #10 a=1; b=1; c=0; d=0;
    #10 a=1; b=1; c=0; d=1;
    #10 a=1; b=1; c=1; d=0;
    #10 a=1; b=1; c=1; d=1;
    $finish;
end

endmodule

```


OUTPUT:

 

Structural level:

```
module logic_function (output, a, b, c, d);
```

```
input a, b, c, d;
```

```
output y
```

```
wire w1, w2, w3, w4, w5, w6;
```

```
nand g1(w1, a, b);
```

```
and g2(w2, c, d);
```

```
or g3(w3, w1, w2);
```

```
nand g4(w4, c, d);
```

```
and g5(w5, a, b);
```

```
or g6(w6, w4, w5);
```

```
xor g7(y, w3, w6);
```

```
endmodule
```

Task4 Solution:

Verilog RTL code:

```
module lab2_4;
reg a1=0;
reg b1=1;

always begin
    #1 a1 = ~a1;
end
always begin
    #2 b1 = ~b1;
end

initial begin
    $dumpfile("l.vcd");
    $dumpvars;
    #100 $finish;
end

endmodule
```

OUTPUT:

