

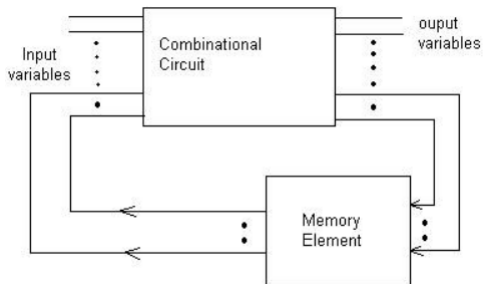


- **Sequential Circuits:**
- **Present I/P + Previous O/P = Present O/p.**
- **Feedback**
- **Memory**
- **Examples:**
- **FF, Registers, Counters etc.**

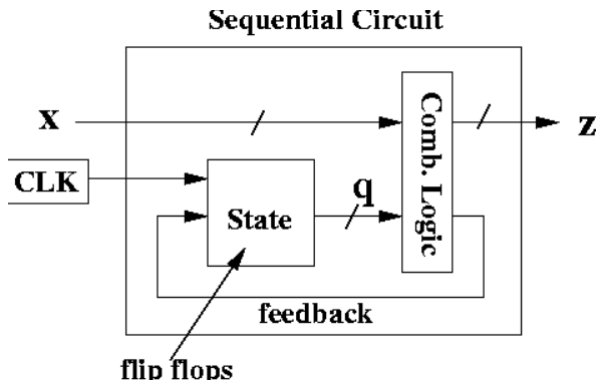- **Real life applications:**
- **Traffic light controller:**
- **Color: Green or Red.**
- **Rocket Launcher: Series of actions.**
- **Elevator: Remembering the no. of floor's.**



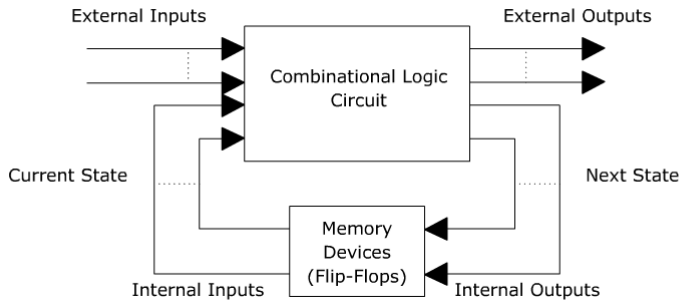




- **Figure is theoretical model of sequential circuit with**
- **combinational logic and some storage elements.**
- **There are two types of input to the combinational logic:**
- **External:**
- **Internal:**


Feedback

- Feedback is when either part -or- full output is given back to the input, for further processing.
- Feedback can be positive (e.g., oscillators) or negative (e.g., amplifiers) in terms of values.
- Important:
The forward path in the circuit should be a function in order to have a meaningful feedback mechanism.


Types of sequential logic circuits

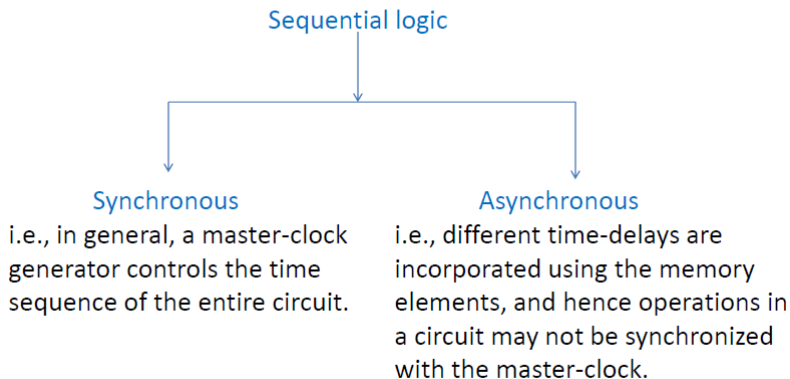

- **Synchronous:**

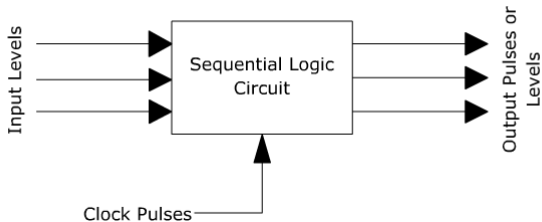

- **Asynchronous:**

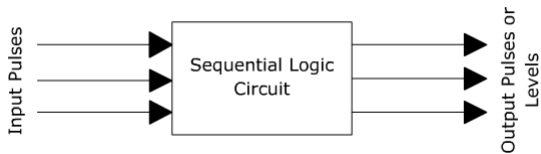


Clocked sequential circuits

- Sequential circuits that use clock pulses in the inputs of the memory elements are called clocked sequential circuits.
- Most frequently used types of sequential logic.
- The memory elements used in such circuits are called *flip-flops*.

Flip-flop

- Binary cells capable of storing **one bit of information**, as long as power is deliver to them.
- **Two outputs:**
one representing the **normal** value
and the second one representing **it's complemented** value.
- **Inputs:**
number of inputs varies and the ways in which binary information can enter a flip-flop also differ and hence generates different types of flip-flops.


- SR Latch using NOT Gate: ??

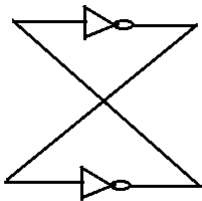

- **NOT Gate: Only one i/p**
- **We need minimum two i/p one for feedback path and other for external i/p**

A basic Flip-flop using NOR gates

Sometimes called as “SR Latch”

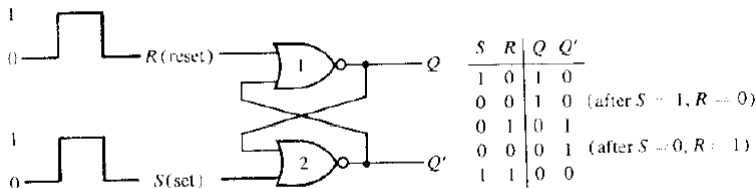


- $S = 1, R = 0, Q = 1$ and $Q' = 0$
- $S = 0, R = 0, Q = 1$ and $Q' = 0$ [Memory State/no change/previous state]
- $S = 0, R = 1, Q = 0$ and $Q' = 1$
- $S = 0, R = 0, Q = 0$ and $Q' = 1$ [Memory State]

- **$R=1$ and $S=0$: To store the 0 in the latch.**
- **We can remove the external i/p.**
- **$R=0$ and $S=1$: To store the 1 in the latch.**

- $S = 1, R = 1, Q = 0$ and $Q' = 0$ [invalid condition]
- $S = 0, R = 0, Q = 1$ and $Q' = 0$ [MS] [upper Gate o/p first]
- $S = 0, R = 0, Q = 0$ and $Q' = 1$ [MS] [Lower Gate o/p first]
- Not reliable circuit.

A basic Flip-flop using NAND gates

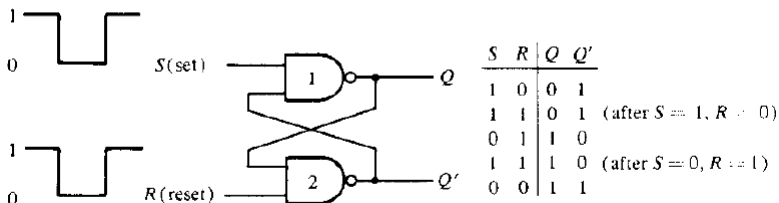

- $S = 1, R = 0, Q = 0$ and $Q' = 1$
- $S = 1, R = 1, Q = 0$ and $Q' = 1$ [Memory State/no change/previous state]
- $S = 0, R = 1, Q = 1$ and $Q' = 0$
- $S = 1, R = 1, Q = 1$ and $Q' = 0$ [Memory State]

- **$R=1$ and $S=0$: To store the 1 in the latch.**
- **We can remove the external i/p.**
- **$R=0$ and $S=1$: To store the 0 in the latch.**

- $S = 0, R = 0, Q = 1$ and $Q' = 1$ [invalid condition]
- $S = 1, R = 1, Q = 0$ and $Q' = 1$ [MS] [upper Gate o/p first]
- $S = 1, R = 1, Q = 1$ and $Q' = 0$ [MS] [Lower Gate o/p first]
- Not reliable circuit.