




# Test Bench

**Dr. Yash Agrawal**  
Visiting Faculty, IIT Vadodra  
Associate Professor, DA-IICT Gandhinagar


## Functionality Module

### Anatomy of a Module in Verilog HDL

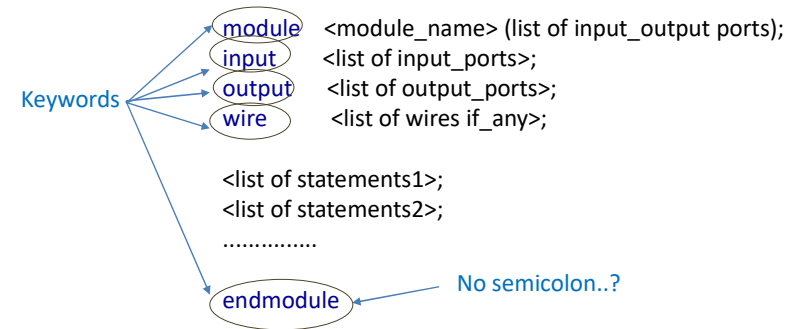

## Test Bench

### Anatomy of Test Bench

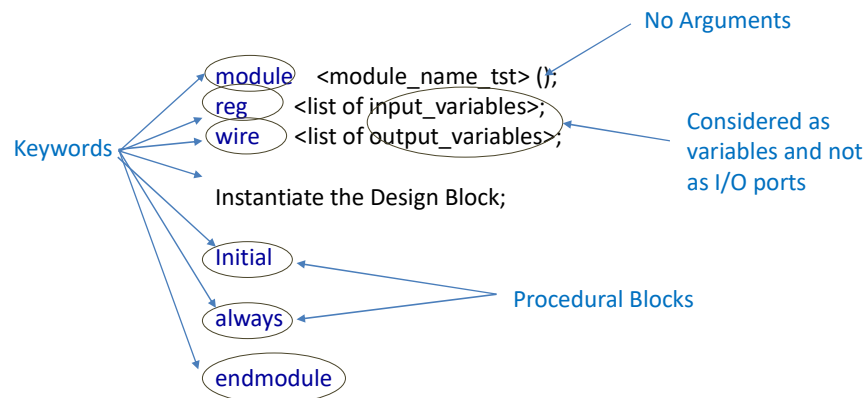

## Contd...

### Test Bench Application

- To check functionality of module (provide test values to the system).
- To generate signals.


Contd...

## Test Bench Application

- To check functionality of module (provide test values to the system).
- To generate signals.

Contd...

## Test Bench: Half Adder and Test Bench

 

### Test Bench1


```
module half_adder (s, c, a, b);
input a, b;
output s, c;
assign s = a ^ b;
assign c = a & b;
endmodule
```

```
t=0 s1 = 1'b0; c1 = 1'b0;
t=2 s1 = 1'b1; c1 = 1'b0;
t=4 s1 = 1'b1; c1 = 1'b0;
t=6 s1 = 1'b0; c1 = 1'b1;
```

```
module half_adder_tst1 ();
reg a1, b1;
wire s1, c1;
half_adder h1(s1, c1, a1, b1);
initial
begin
#0 a1 = 1'b0; b1 = 1'b0;
#2 a1 = 1'b0; b1 = 1'b1;
#2 a1 = 1'b1; b1 = 1'b0;
#2 a1 = 1'b1; b1 = 1'b1;
end
endmodule
```

Contd...

## Test Bench: Half Adder and Test Bench

 

### Test Bench2 (using Vector Notation)


```
module half_adder (s, c, a, b);
input a, b;
output s, c;
assign s = a ^ b;
assign c = a & b;
endmodule
```

```
t=0 s1 = 1'b0; c1 = 1'b0;
t=2 s1 = 1'b1; c1 = 1'b0;
t=4 s1 = 1'b1; c1 = 1'b0;
t=6 s1 = 1'b0; c1 = 1'b1;
```

```
module half_adder_tst2 ();
reg [1:0] M;
wire s1, c1;
half_adder h1(s1, c1, M[0], M[1]);
initial
begin
#0 M[0] = 1'b0; M[1] = 1'b0;
#2 M[0] = 1'b0; M[1] = 1'b1;
#2 M[0] = 1'b1; M[1] = 1'b0;
#2 M[0] = 1'b1; M[1] = 1'b1;
end
endmodule
```

Contd...

## Test Bench: Half Adder and Test Bench

 

### Test Bench3 (using Hierarchy Notation)


```
module half_adder (s, c, a, b);
input a, b;
output s, c;
assign s = a ^ b;
assign c = a & b;
endmodule
```

```
t=0 s1 = 1'b0; c1 = 1'b0;
t=2 s1 = 1'b1; c1 = 1'b0;
t=4 s1 = 1'b1; c1 = 1'b0;
t=6 s1 = 1'b0; c1 = 1'b1;
```

```
module half_adder_tst3 ();
reg a1, b1;
wire s1, c1;
half_adder h1(.s(s1), .c(c1), .a(a1), .b(b1));
initial
begin
#0 a1 = 1'b0; b1 = 1'b0;
#2 a1 = 1'b0; b1 = 1'b1;
#2 a1 = 1'b1; b1 = 1'b0;
#2 a1 = 1'b1; b1 = 1'b1;
end
endmodule
```

Contd...

## Test Bench: Half Adder and Test Bench

 

Test Bench4 (using Concatenation Operator)

```


module half_adder (s, c, a, b);
input a, b;
output s, c;
assign s = a ^ b;
assign c = a & b;
endmodule

module half_adder_tst4 ();
reg a1, b1;
wire s1, c1;
half_adder h1(s1, c1, a1, b1);
initial
begin
#0 {a1, b1} = {1'b0, 1'b0};
#2 {a1, b1} = {1'b0, 1'b1};
#2 {a1, b1} = {1'b1, 1'b0};
#2 {a1, b1} = {1'b1, 1'b1};
end
endmodule

```

Contd...
 
## 1. Test Bench: 2-bit 2-input Half Adder



Test Bench

```


module half_adder (s, c, a, b);
input [1:0] a, b;
output [1:0] s, c;
assign s = a ^ b;
assign c = a & b;
endmodule

module half_adder_tst1 ();
reg [1:0] a1, b1;
wire [1:0] s1, c1;
half_adder h1(s1, c1, a1, b1);
initial
begin
#0 a1 = 2'b00; b1 = 2'b00;
#2 a1 = 2'b00; b1 = 2'b10;
#2 a1 = 2'b10; b1 = 2'b00;
#2 a1 = 2'b10; b1 = 2'b10;
end
endmodule

```

Contd...
 
## 2. Test Bench: 2-bit Module; 1-bit Test Bench



Test Bench

```


module half_adder (s, c, a, b);
input [1:0] a, b;
output [1:0] s, c;
assign s = a ^ b;
assign c = a & b;
endmodule

module half_adder_tst1 ();
reg a1, b1;
wire s1, c1;
half_adder h1(s1, c1, a1, b1);
initial
begin
#0 a1 = 1'b0; b1 = 1'b0;
#2 a1 = 1'b0; b1 = 1'b1;
#2 a1 = 1'b1; b1 = 1'b0;
#2 a1 = 1'b1; b1 = 1'b1;
end
endmodule

```

Contd...
 
## 3. Test Bench: 1-bit Module; 2-bit Test Bench



Test Bench

```

module half_adder (s, c, a, b);
input a, b;
output s, c;
assign s = a ^ b;
assign c = a & b;
endmodule

module half_adder_tst1 ();
reg [1:0] a1, b1;
wire [1:0] s1, c1;
half_adder h1(s1, c1, a1, b1);
initial
begin
#0 a1 = 2'b00; b1 = 2'b00;
#2 a1 = 2'b00; b1 = 2'b10;
#2 a1 = 2'b10; b1 = 2'b00;
#2 a1 = 2'b10; b1 = 2'b10;
end
endmodule

```

Contd...


#### 4. Test Bench: 1-bit Module; 2-bit Test Bench

```
module half_adder (s, c, a, b);
input a, b;
output s, c;
assign s = a ^ b;
assign c = a & b;
endmodule
```

```
t=0 s1 = 2'bz0; c1 = 2'bz0;
t=2 s1 = 2'bz1; c1 = 2'bz0;
t=4 s1 = 2'bz1; c1 = 2'bz0;
t=6 s1 = 2'bz0; c1 = 2'bz1;
```
 
##### Test Bench

```
module half_adder_tst1 ();
reg [1:0] a1, b1;
wire [1:0] s1, c1;
half_adder h1(s1, c1, a1, b1);
initial
begin
#0 a1 = 2'b00; b1 = 2'b00;
#2 a1 = 2'b00; b1 = 2'b01;
#2 a1 = 2'b01; b1 = 2'b00;
#2 a1 = 2'b01; b1 = 2'b01;
end
endmodule
```



Contd...


#### 5. Test Bench: 1-bit Module; 2-bit Test Bench

```
module half_adder (s, c, a, b);
input [1:0] a, b;
output [1:0] s, c;
assign s = a ^ b;
assign c = a & b;
endmodule
```

```
t=0 s1 = 2'b00; c1 = 2'b00;
t=2 s1 = 2'b01; c1 = 2'b00;
t=4 s1 = 2'b01; c1 = 2'b00;
t=6 s1 = 2'b00; c1 = 2'b01;
```
 
##### Test Bench

```
module half_adder_tst1 ();
reg [1:0] a1, b1;
wire [1:0] s1, c1;
half_adder h1(s1, c1, a1, b1);
initial
begin
#0 a1 = 1'b0; b1 = 1'b0;
#2 a1 = 1'b0; b1 = 1'b1;
#2 a1 = 1'b1; b1 = 1'b0;
#2 a1 = 1'b1; b1 = 1'b1;
end
endmodule
```



Contd...


#### Concept of `timescale

```
module half_adder (s, c, a, b);
input a, b;
output s, c;
assign s = a ^ b;
assign c = a & b;
endmodule
```

```
t=0 s1 = 1'b0; c1 = 2'b0;
t=3ps s1 = 1'b1; c1 = 2'b0;
t=7ps s1 = 1'b1; c1 = 2'b0;
t=11ps s1 = 1'b0; c1 = 2'b1;
```
 
##### Test Bench


```
module half_adder_tst2 ();
reg a1, b1;
wire s1, c1;
half_adder h1(s1, c1, a1, b1);
initial
begin
#0 a1 = 1'b0; b1 = 1'b0;
#0.003 a1 = 1'b0; b1 = 1'b1;
#0.0044 a1 = 1'b1; b1 = 1'b0;
#0.0037 a1 = 1'b1; b1 = 1'b1;
end
endmodule
```



Contd...
 
#### Test Bench Application

- To check functionality of module (provide test values to the system).
- To generate signals.



## Test Bench using 'always' Block

```
module half_adder (s, c, a, b);
input a, b;
output s, c;
assign s = a ^ b;
assign c = a & b;
endmodule
```

## Test Bench1

```
module half_adder_tst3 ();
reg a1, b1;
wire s1, c1;
half_adder h1(s1, c1, a1, b1);

initial
begin
#0 a1 = 1'b1; b1 = 1'b1;
end

always
#2 b1 = ~b1;

always
#4 a1 = ~a1;

endmodule
```

## Test Bench2

```
module half_adder_tst4 ();
reg a2, b2;
wire s2, c2;
half_adder h2(s2, c2, a2, b2);

initial
begin
#0 a2 = 1'b1; b2 = 1'b1;
end

always
begin
#2 b2 = ~b2;
#4 a2 = ~a2;
end

endmodule
```

## Test Bench using 'always' Block

## Test Bench1

```
module half_adder_tst3 ();
reg a1, b1;
wire s1, c1;
half_adder h1(s1, c1, a1, b1);

initial
begin
#0 a1 = 1'b1; b1 = 1'b1;
end

always
#2 b1 = ~b1;

always
#4 a1 = ~a1;

endmodule
```

## Test Bench2

```
module half_adder_tst4 ();
reg a2, b2;
wire s2, c2;
half_adder h2(s2, c2, a2, b2);

initial
begin
#0 a2 = 1'b1; b2 = 1'b1;
end

always
begin
#2 b2 = ~b2;
#4 a2 = ~a2;
end

endmodule
```

