



Indian Institute of Information Technology Vadodra

CS/IT 429

Transistor

Dr. Yash Agrawal
Visiting Faculty, IIIT Vadodra
Associate Professor, DA-IICT Gandhinagar

Transistors

Used as Amplifier (Analog Domain)

Used as Switch (Digital Domain)

Dr. Yash Agrawal @ IIIT Vadodra

2

Amplifiers

What is Amplification...?





Dr. Yash Agrawal @ IIIT Vadodra

3

Amplifiers


What is Amplification...?

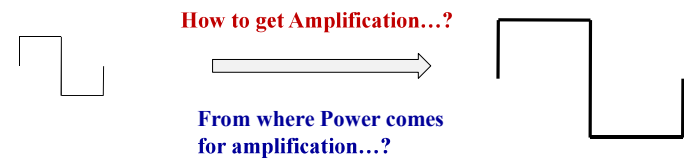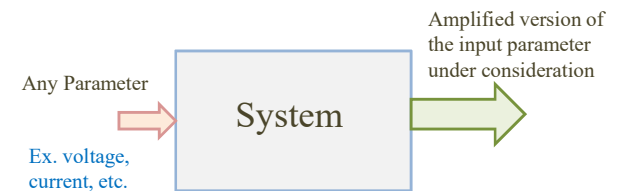


Dr. Yash Agrawal @ IIIT Vadodra

4

Amplifiers

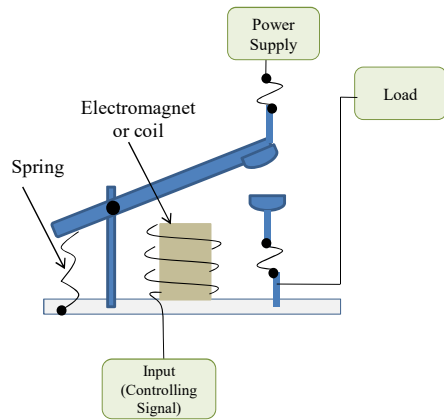


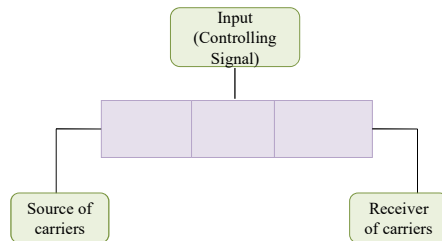Amplification using
Electromechanical Relays




Amplification using
Solid State Devices

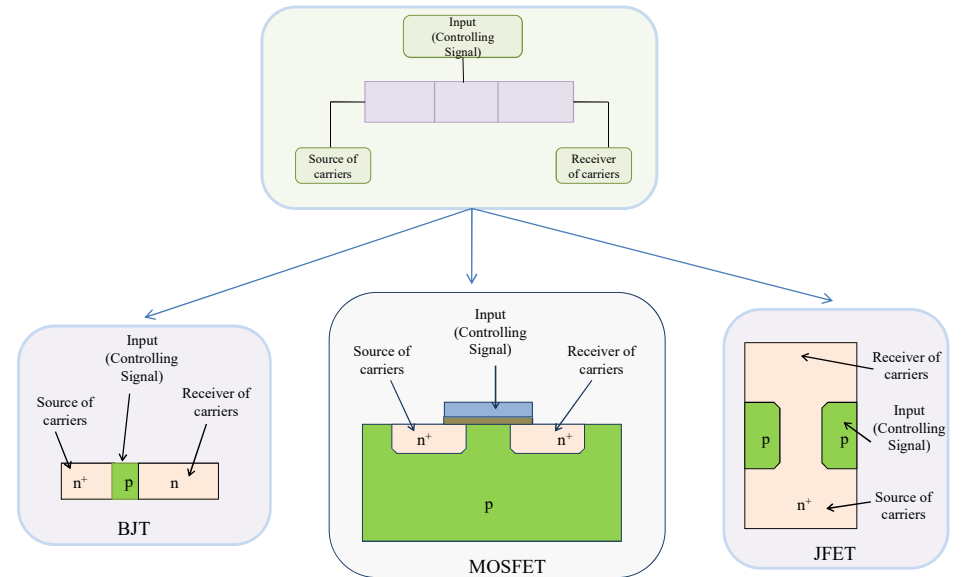Basic Principle of Transistors and a few Examples




MOSFET

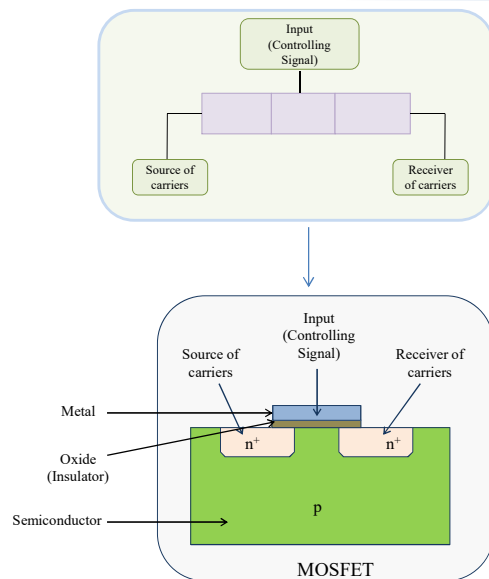


Shape, Symbol and Types....



Enhancement Type

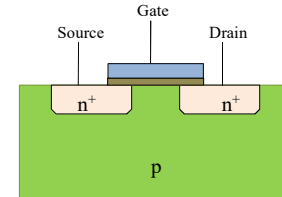





n-channel Enhancement
Type MOSFET

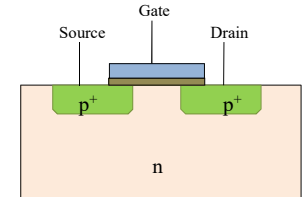




p-channel Enhancement
Type MOSFET

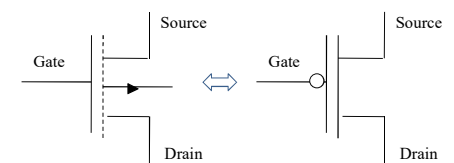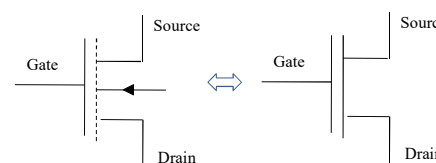

Depletion Type

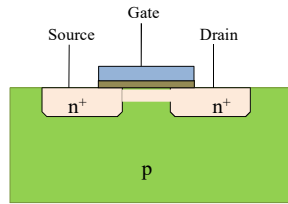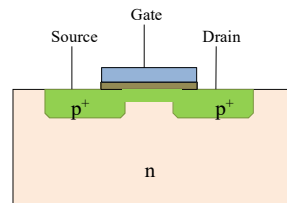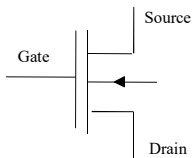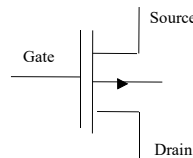n-channel Depletion
Type MOSFETp-channel Depletion
Type MOSFET

MOS Transistors as Switch

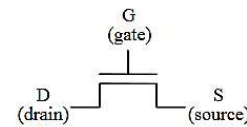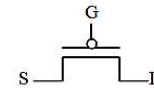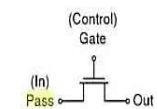*n*MOS transistor:Closed (conducting) when
Gate = 1 (V_{DD})Open (non-conducting) when
Gate = 0 (ground, 0V)*p*MOS transistor:Closed (conducting) when
Gate = 0 (ground, 0V)Open (non-conducting) when
Gate = 1 (V_{DD})

Gate	Pass	Out
0	0	hi-Z
0	1	hi-Z
1	0	0
1	1	1

I am available/approachable at

email: yash_agrawal@iiitvadodara.ac.in
yash_agrawal@daiict.ac.in