

Indian Institute of Information Technology – Vadodara

Mid-Semester Examination Autumn 2022-23

B. Tech. (IT & CSE)


EC-201: Digital Logic Design

Time: 2:0 hrs

Max. Marks: 60


Attempt all questions

 - Q.1 Do the followings
- (a) $(110110)_2 = (?)_{10}$ 2
- (b) For function $AB+AB'C+AB'C'$, find the minimum no. of NAND Gates? 2
- (c) Minimize the logical expression $(A+B+C)(A+B'+C)(A+B+C')$ using Boolean theorems. 2
- (d) Identify and remove the redundant term from the logical expression $AB+A'C+BC$ 2
- (e) Minimize the function using K-Map $f(A,B) = \sum m(0,2,3)$. 2
- Q.2 (a) Implement the full subtractor circuit using minimum number of NAND gate only. 5
- (b) Explain carry look ahead adder with suitable diagram and drive the expression for it. 5
- Q.3 (a) Minimize the function using K-Map $f(A,B,C,D) = \sum m(0,1,2,3,5,7,9,10,11,13,15)$ 5
- (b) Take your roll number and write it in the 4-variable SOP function (for eg. If roll no is 201411012 the SOP function will be $f(A,B,C,D) = \sum m(2, 0, 1, 4, 1, 1, 0, 1, 2) = \sum m(0, 1, 2, 4)$. And also take don't care conditions for 10, 11, 12, 13, 14, 15. Now make its 4-variable K-map. And implement it using basic Gates only. 5
- Q.4 (a) Find the output f of the following circuit. 5




- (b) Consider the two cascaded 2-to-1 multiplexers as shown in the 5

figure. The minimal sum of products form of the output X is ?

 

Q. 5

 - (a) The below sequential circuit is design using JK flip-flops is initialized with $Q_2 Q_1 Q_0 = 000$. The state sequence for this circuit for the next 5th clock cycle is? 5



001 - 1
010 - 1
011 - 2
100 - 1
101 - 2


5

- (b) Convert the S-R flip flop using J-K flip flop.

Q. 6

- (a) Design a circuit that accept binary numbers between 1 & 5 and generates an output, equals to the numbers of 1's in the input. Use only 2-input logic gates for implementation. **(5 Marks)**

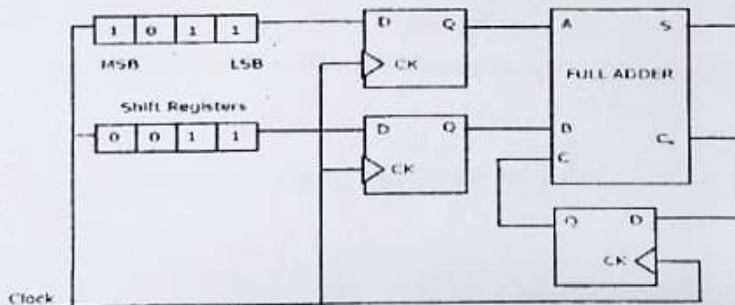- (b) The circuit shown in figure below, two 4-bit parallel-in serial-out shift registers loaded with the data shown are used to feed the data to a full adder. Initially, all the flip-flops are in clear state. After applying two clock pulses, find out the outputs of the full-adder S and C0. **(5 Marks)**



000 - m0
001 - m1
010 - m2
011 - m3
100 - m4
101 - m5
110 - m6
111 - m7

*****END*****

