

Started on Saturday, 8 October 2022, 11:00 AM

State Finished

Completed on Saturday, 8 October 2022, 11:05 AM

Time taken 4 mins 58 secs

Marks 2.00/5.00


Grade 4.00 out of 10.00 (40%)

Question 1

Complete

Mark 1.00 out of 1.00

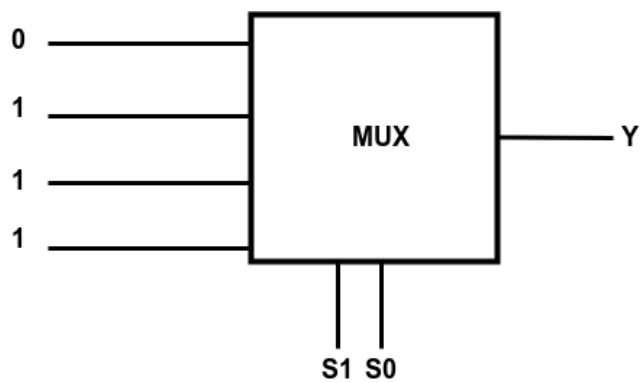The out Y of the circuit given below will perform the function of ?




- ☐ a. X-OR Gate
- ☐ b. X-NOR Gate
- ☒ c. OR Gate
- ☐ d. AND Gate

Question 2

Complete

Mark 0.00 out of 1.00

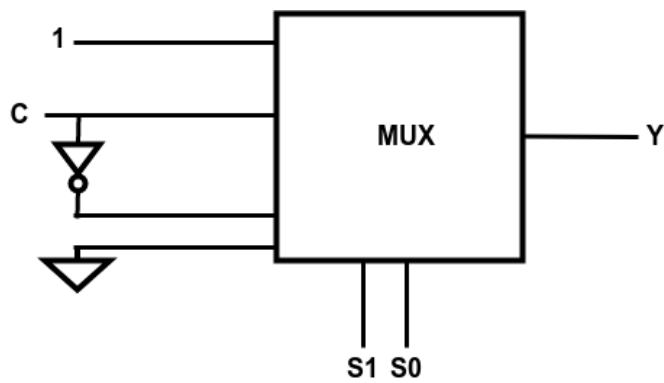What is the output of the circuit given below? If $S1 = A$ and $S0 = B$




- ☐ a. $A'B + ABC + AB'C'$
- ☒ b. $AB + A'BC + AB'C'$
- ☐ c. $A'B + A'BC + A'B'C'$
- ☐ d. $A'B' + A'BC + AB'C'$

Question **3**

Complete

Mark 1.00 out of 1.00

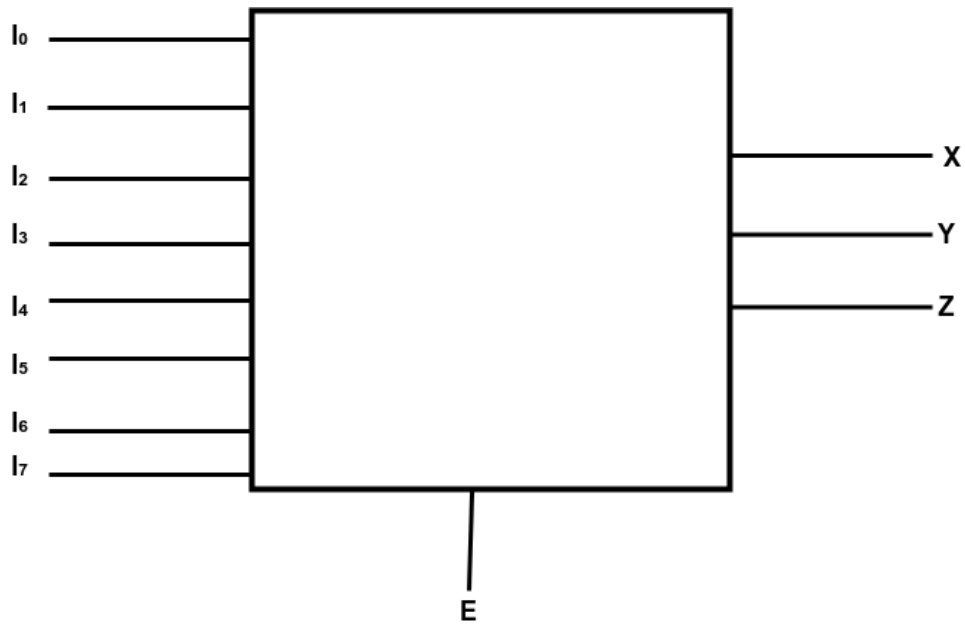Choose the right option for the circuit given below?




- ☐ a. Octal to Hexadecimal Decoder
- ☐ b. Decimal to BCD Decoder
- ☒ c. Octal to Binary Decoder
- ☐ d. Decimal to Binary Decoder

Question 4

Complete

Mark 0.00 out of 1.00

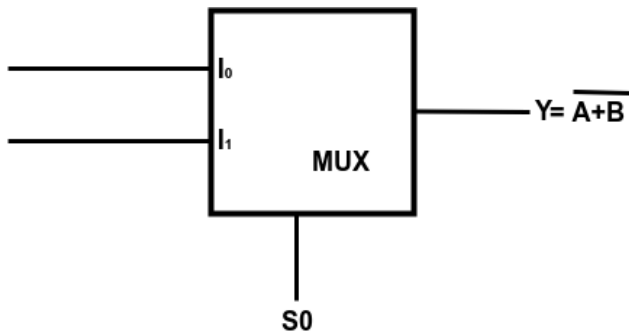For the circuit given below choose the correct option?



- ☒ a. $S_0 = A$ and $I_0 = I_1 = B'$
- ☐ b. $S_0 = A$, $I_0 = B'$ and $I_1 = 0$
- ☐ c. $S_0 = A$, $I_0 = B$ and $I_1 = 1$
- ☐ d. $S_0 = A$, $I_0 = 0$ and $I_1 = 1$

Question 5

Complete

Mark 0.00 out of 1.00

Minimum numbers of NAND Gates requires to implements the $X + XY'Z$?

- ☐ a. 1
- ☐ b. 3
- ☐ c. 0
- ☒ d. 2

[◀ Announcements](#)

EC-201-Test-II-05-11-2022_11am ▶