



# Indian Institute of Information Technology Vadodara

Mid-Semester-Examination-Autumn-2024-25

Specialization: B. Tech. (IT & CSE)

Course Code: EC-201 (Digital Logic Design)

Time: 2.0 Hours

MM: 60

Read the instructions carefully.

- ☐ Attempt ALL the questions.
- ☐ Make point wise answers for the required part.

**Question 1: ( 2+2+2+2+2=10 Points)**

State whether the following statements are TRUE [T] or FALSE [F] and write a few lines to justify your answer.

- ✓ (a) Moore's Law related to the speed of electrons in a VLSI chip?
- ✓ (b)  $F(w, x, y, z) = \sum m(0, 1, 2, 3, 7, 8, 10) + \sum d((5, 6, 11, 15))$  is POS form?
- (c) The minimum number of 2-input NAND gates required to implement a Full Adder are 10.
- ✓ (d) Flip flop is edge sensitive and latch is level sensitive.
- (e) Lower execution time of any logic circuit can be achieved by using the minimized logical expression.

**Question 2: ( 2+2+2+2+2=10 Points)**

- (a) Prove that  $A \oplus B \oplus AB = A + B$
- ✓ (b) Convert binary code 1001 into gray code.
- (c) Find the 1's and 2's complement of the binary number 111101.
- (d) What will be the BCD sum of  $A = (184)_{10}$  and  $B = (576)_{10}$ ?
- (e) Perform a binary subtraction of  $A = 10011$  and  $B = 11101$ .


**Question 3: ( 2+2+2+2+2=10 Points)**

- ✓ (a)  $F(A, B, C) = ABC + A'B'C + ABC'$ , find the minimum numbers of NAND gates required to implement the function.
- (b) Simplify the function  $F(A, B, C) = A'B + AC + BC$  redundant theorem.
- (c) Implement the half subtractor circuit by using the minimum number of NAND gates.
- (d) Minimize the function  $F(A, B, C) = \sum m(0, 1, 6, 7) + \sum d(3, 4, 5)$  using K-map.
- (e) Minimize the function  $F(A, B, C, D) = A' + AB' + ABC'$  using K-map.




Q. 4

 - (a) The logic function implemented by the circuit below is (ground implies logic 0)? Give the optimized solution. 5




 - (a) The sequence of states  $(Q_1, Q_0)$  of the given is? Give a step by step solution for the circuit. 5



Q. 5

 - (a) Analyze the circuit containing D flip-flops shown below by giving the value for Q1 and Q2 that result from each clock trigger. The flip-flops are positive-edge triggered so the question will ask about the values at the negative edges, by which time the flip-flop outputs should have settled. At time  $t=0$ ,  $Q1=0$  and  $Q2=0$ . Note that the flip-flops are commonly-clocked. 5



- (b) A 4-bit priority encoder has inputs  $D_3, D_2, D_1$  and  $D_0$  in descending order of priority. The two-bit output AB is generated as 00, 01, 10, and 11 corresponding to inputs  $D_3, D_2, D_1$  and  $D_0$ , respectively. The Boolean expression of the output bit B is..... 5

Q. 6

- (a) Define race around condition. How to remove race around conditions? 5  
 (b) Design a 3-bit asynchronous up-counter. Draw the output diagram/Timing Diagram. 5  
 (c) Convert S-R flip-flop to J-K flip-flop and draw the state diagram of S-R flip-flop and J-K flip-flop. 5  
 (d) Define Ring counter and Johnson counter and find usable states and no unusable states. 5  
 (e) Implement half adder using 2x4 Decoder. 5

.....END.....