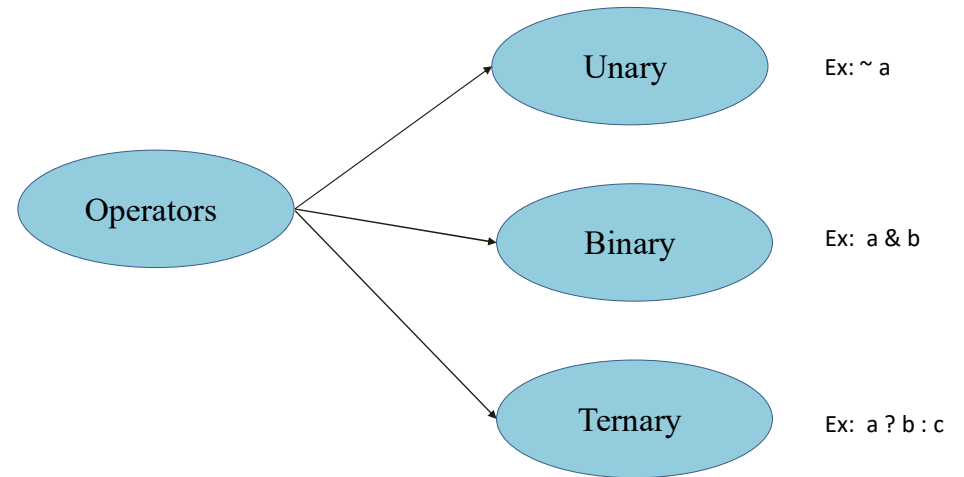




# Operators

**Dr. Yash Agrawal**  
Visiting Faculty, IIIT Vadodara  
Associate Professor, DA-IICT Gandhinagar

## Introduction



## Operators

- Arithmetic
- Bitwise
- Logical
- Reduction
- Relational and Equality
- Shift
- Concatenate and Replication
- Conditional

## Operators

### Arithmetic Operator

- Addition ( + )
- Subtraction ( - )
- Multiplication ( \* )
- Division ( / )
- Modulus ( % )
- Power/Exponent ( \*\* )

If any input to arithmetic operator is x, it leads to output as x


# Operators

## Arithmetic Operator

Example

1. To Check: Whether the output is even or odd

- A and B can be considered as 3 bits

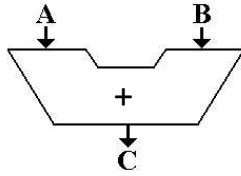

2. Check:  $(a + b)^3 = a^3 + b^3 + 3a^2b + 3ab^2$

- Use Only Arithmetic Operators
- a and b can be considered as 2 bits

# Operators

## Bitwise Operator

- Unary NOT ( ~ )
- Binary AND ( & )
- Binary OR ( | )
- Binary XOR ( ^ )
- Binary XNOR ( ~ ^ or ^ ~ )

- Bitwise operator performs bit-by-bit operation on two operands.

- z is treated as x in bitwise operation.


# Operators

## Bitwise Operator

Example


Implement Full Adder using bitwise operator

- Inputs can be considered as single bit

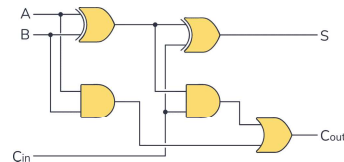

Implement using Bit-wise Operator

- Inputs can be considered as single bit

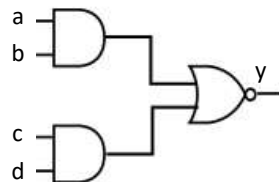

# Operators

## Logical Operator

- Logical NOT ( ! )
- Logical AND ( && )
- Logical OR ( || )

- Only one-bit output.

## Logical Operator

Example

1) If  $a = 5'b11011$   
 $b = 4'b0010$

If  $a \&\& b = 1 \&\& 1 = 1$   
 $a || b = 1 || 1 = 1$   
 $!a = \text{not (logical 1)} = 0$   
 $!b = \text{not (logical 1)} = 0$

2) If  $a = 5'b11011$   
 $b = 4'b0000$

If  $a \&\& b = 1 \&\& 0 = 0$   
 $a || b = 1 || 0 = 1$   
 $!a = \text{not (logical 1)} = 0$   
 $!b = \text{not (logical 0)} = 1$

## Logical Operator

Example

3) If  $a = 4'd3$   
 $b = 5'd0$


If  $a \&\& b = 1 \&\& 0 = 0$   
 $a || b = 1 || 0 = 1$   
 $!a = \text{not (logical 1)} = 0$   
 $!b = \text{not (logical 0)} = 1$

4) If  $a = 2'b0x$   
 $b = 2'b10$


If  $a \&\& b = x \&\& 1 = x$   
 $a || b = x || 1 = 1$   
 $!a = \text{not (logical x)} = x$   
 $!b = \text{not (logical 1)} = 0$

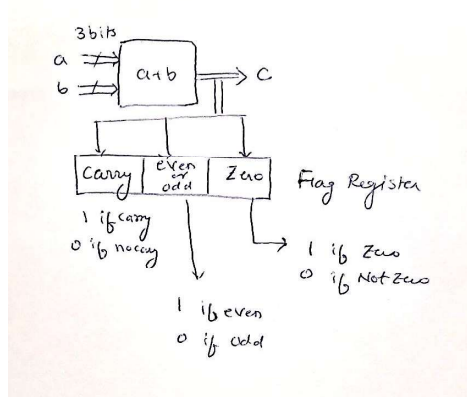Example

Write the HDL code for the circuit defined



Example

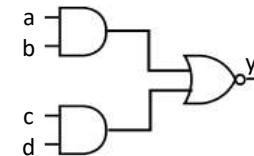

```
module aoi1 (y, a, b, c, d);
input [3:0] a, b, c, d;
output [3:0] y;
assign y = ~((a & b) | (c & d));
endmodule
```

```
module aoi2 (y, a, b, c, d);
input [3:0] a, b, c, d;
output [3:0] y;
assign y = !((a && b) | (c && d));
endmodule
```

$a = 4'b0001$   
 $b = 4'b0000$   
 $c = 4'b1110$   
 $d = 4'b1001$



Identify the output values...!

# Operators

## Reduction Operator


- Reduction AND ( & )
- Reduction OR ( | )
- Reduction NAND ( ~ & )
- Reduction NOR ( ~ | )
- Reduction XOR ( ^ )
- Reduction XNOR ( ~ ^ or ^ ~ )

- Reduction operators take one operand and returns a single bit.

# Operators

## Example

Single parity check bit

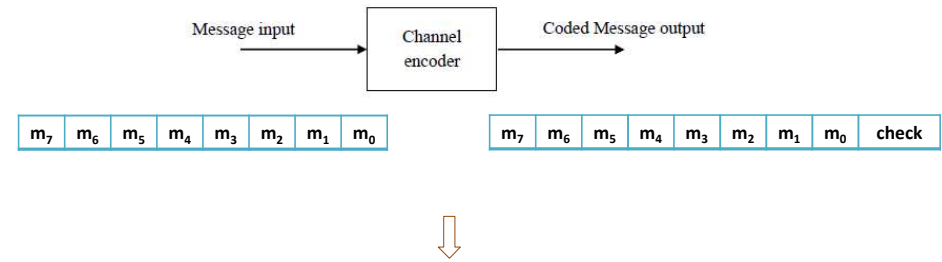

Implement the functionality defined above...

# Operators

## Bitwise, Logical and Reduction Operators

Operators		
Bitwise	Logical	Reduction
Not ( ~ )	NOT ( ! )	
AND ( & )	AND ( && )	AND ( & )
OR (   )	OR (    )	OR (   )
EXOR ( ^ )		EXOR ( ^ )
EXNOR ( ~^ or ^~ )		EXNOR ( ~^ or ^~ )
		NAND ( ~& )
		NOR ( ~  )

# Operators

## Relational and Equality Operator

### Relational Operator

- Less than ( < )
- Less than or equal to ( <= )
- Greater than ( > )
- Greater than or equal to ( >= )

- If z or x, return x value.

## Relational Operator

Example

```
1) If a = 4
    b = 3
    c = 4'b1010
    d = 4'b1101
    e = 4'b1xxx
```

```
a <= b    = 0
a > b     = 1
c >= d    = 0
c < d     = x
```

## Relational Operator

Example

Find whether a is greater than or equal to b using Verilog HDL

- Inputs – 'a' and 'b' can be considered as 3 bits



Implement the functionality defined above...

## Relational and Equality Operators

### Equality Operator

- Equality ( == ) // Possible logical values are 0, 1, x
- Inequality ( != ) // Possible logical values are 0, 1, x
- Case Equality ( === ) // Possible logical values are 0, 1
- Case Inequality ( !== ) // Possible logical values are 0, 1

## Equality Operator

Example

Implement a system to compare two numbers

- Inputs – 'a' and 'b' can be considered as 8 bits

```
module compare2 (a, b, check1, check2);
    input [7:0] a, b;
    output check1, check2;

    assign check1 = a == b;
    assign check2 = a === b;
endmodule
```



Identify the output values...!

# Operators

## Equality Operator


Example

Implement a system to compare two numbers

- Inputs – 'a' and 'b' can be considered as 8 bits



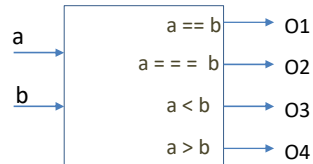Implement the functionality defined above...



# Operators

## Shift Operator

Example


Implement divide by 4 Operation

- Input – 'dividend' be considered as 4 bits



Implement Multiply by 2 and Multiply by 4 Operations

- Input – 'in' be considered as 3 bits

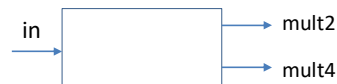

# Operators

## Shift Operator

- Shift Left ( << )
- Shift Right ( >> )
- Arithmetic Shift Left ( <<< )
- Arithmetic Shift Right ( >>> )

# Operators

## Concatenation and Replication Operators

- Concatenation ( { } )
- Replication ( { { } } )

## Concatenation Operator


Example

`{1'b1, {2 {1'b0}}}` = `3'b100`

If <code>a = 1'b1</code>	<code>Y = {b, c}</code>	<code>Y = 4'b0010</code>
<code>b = 2'b00</code>	<code>Y = {a, b, c, d, 3'b001}</code>	<code>Y = 11'b10010100001</code>
<code>c = 2'b10</code>	<code>Y = {a, b[0], c[1]}</code>	<code>Y = 3'b101</code>
<code>d = 3'b100</code>		

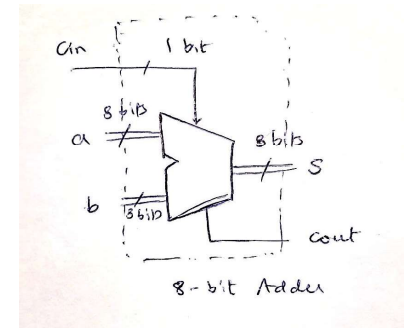Example

Write the HDL code for the circuit defined



Implement the functionality defined above...

## Replication Operator

Example

`{1'b1, {2 {1'b0}}}` = `3'b100`

If <code>a = 1'b1</code>	<code>Y = {4 {a}}</code>	<code>Y = 4'b1111</code>
<code>b = 2'b00</code>	<code>Y = {4 {a}, 2 {b}}</code>	<code>Y = 8'b11110000</code>
<code>c = 2'b10</code>	<code>Y = {4 {a}, 2 {b}, c}</code>	<code>Y = 10'b1111000010</code>
<code>d = 3'b100</code>		

## Conditional Operator

- Conditional ( ? : )

Syntax

Output = Conditional Exp ? True Exp : False Exp;

- If the result is x (ambiguous), then both true\_exp and false\_exp are evaluated bit-by-bit to return for each bit position as
  - o x if the bits are different and
  - o the value of bits if they are same.


# Operators

## Conditional Operator
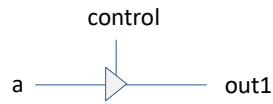
### Example

To model functionality of Tristate Buffer

- Input – 'a' can be considered as 8 bits



Implement the functionality defined above...

# Operators

### Example

```
module logic_condn (a, b, control, out1);  
  input [7 : 0] a, b;  
  input control;  
  output [7 : 0] out1;  
  assign out1 = control ? a : b;  
endmodule
```

a = 8'b1101\_1001  
b = 8'b1000\_0111



Identify the output values...!

# Operators

### Example

Implement 2:1 Mux



- Inputs – 'a' and 'b' can be considered as single bit

Implement 2:1 Mux

- Inputs – 'a' and 'b' to be considered as 8 bits

Implement 2:1 Mux

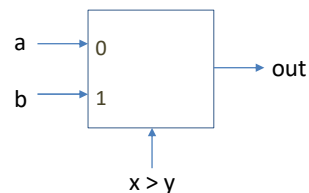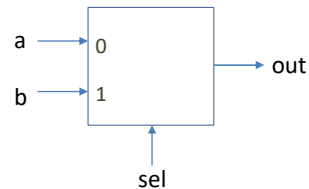- Inputs – 'a' and 'b' can be considered as 8 bits
- 'x' and 'y' can be considered as 3 bits



# Operators

### Example

Find Greatest number amongst 3 numbers: a, b, c

Implement 4:1 Mux using Conditional Operator


- Inputs – 'a', 'b', 'c' and 'd' can be considered as single bit

Implement 4:1 Mux using Bitwise Operator

- Inputs – 'a', 'b', 'c' and 'd' can be considered as single bit

Implement 4:1 Mux using 2:1 Mux Instantiation

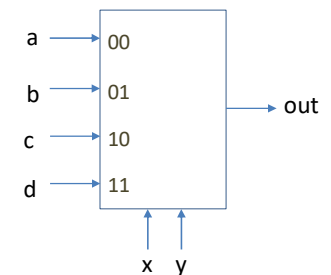- Inputs – 'a', 'b', 'c' and 'd' can be considered as single bit





I am available/approachable at

email: [yash\\_agrawal@iiitvadodara.ac.in](mailto:yash_agrawal@iiitvadodara.ac.in)  
[yash\\_agrawal@daiict.ac.in](mailto:yash_agrawal@daiict.ac.in)